

Topic 9




Register & Shifter

Introduction

- Two major subsystems in typical digital system
 - Controller
 - Controller generates signals to control datapath based on environment event or state
 - Datapath
 - Datapath routes data to particular destination device according to control signals generated by controller
- This chapter introduces numerous datapath components, and simple datapaths


Registers

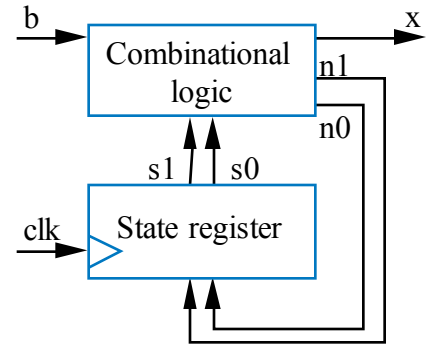  - Can store data, very common in datapaths
- Basic register: Loaded every cycle
 - Useful for implementing FSM -- stores encoded state
 - For other uses, may want to load only on certain cycles





Verilog Modeling of Registers
 
```
module Reg_N_bits (Q, Din, clock);  
    parameter size = 4;  
    input clock;  
    input [size-1:0] Din;  
    output [size-1:0] Q;  
  
    reg Q;  
  
    always @ (posedge clock)  
    begin  
        Q <= Din;  
    end  
endmodule
```



Register with Parallel Load

 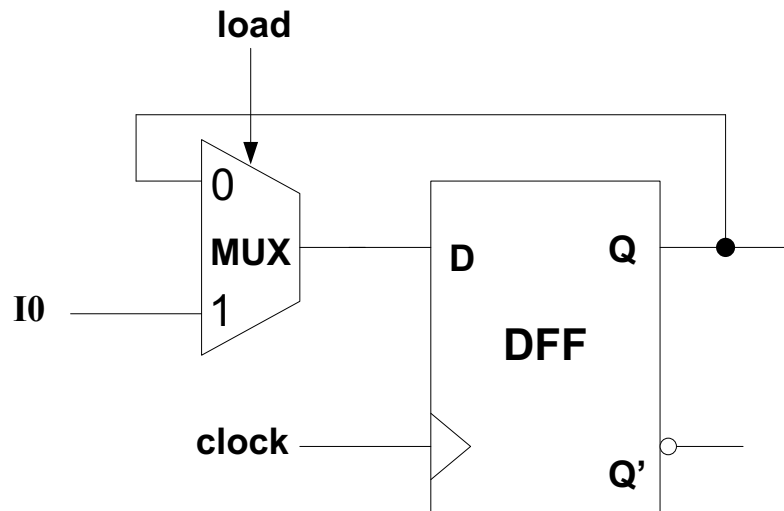
- Add 2x1 mux to each flip-flop
- Register's load input selects mux input to pass
 - Either existing flip-flop value, or new value to load



Synchronous active high Load

Verilog Modeling of Registers
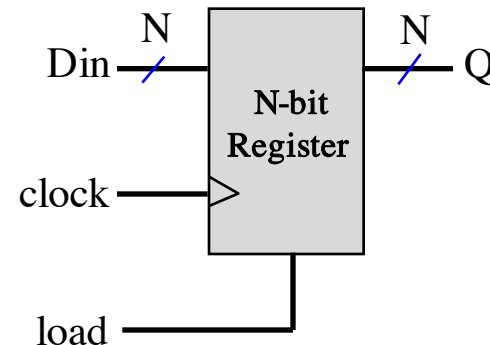
```
module Reg_N_bits (Q, Din, clock, load);  
  parameter size = 4;  
  input clock, load;  
  input [size-1:0] Din;  
  output [size-1:0] Q;  
  
  reg Q;  
  
  always @ (posedge clock)  
  begin  
    if (load) Q <= Din;  
  end  
endmodule
```



Verilog Testbench for Register

```
module Test_Banch;
    parameter half_period = 50;
    parameter reg_size = 3;

    wire [reg_size-1:0] Q;
    reg  [reg_size-1:0] Din;
    reg                      clock, load;


    Reg_N_bits #(reg_size) UUT (Q, Din, clock, load);

    initial begin
        #0    clock = 0; Din = 0;
        #200 Din = 5; load = 1;
        #100 load = 0;
        #200 Din = 3;
        #200 load = 1;
    end

    always #half_period clock = ~clock;


    initial #1000 $stop;
endmodule
```

Timing Diagram from Simulation

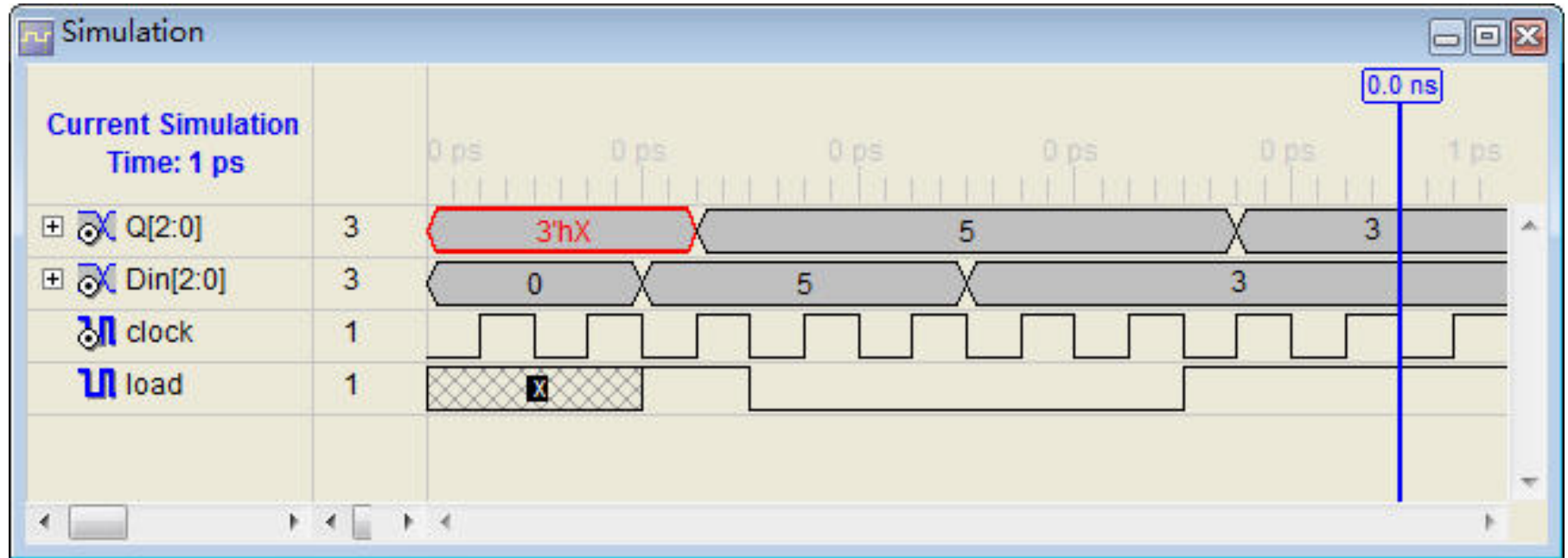


Register Example using the Load Input: Weight Sampler

 
- Scale has two displays
 - Present weight
 - Saved weight
 - Useful to compare present item with previous item
- Use register to store weight
 - Pressing button causes present weight to be stored in register
 - Register contents always displayed as “Saved weight,” even when new present weight appears



Register Example: Above-Mirror Display

 

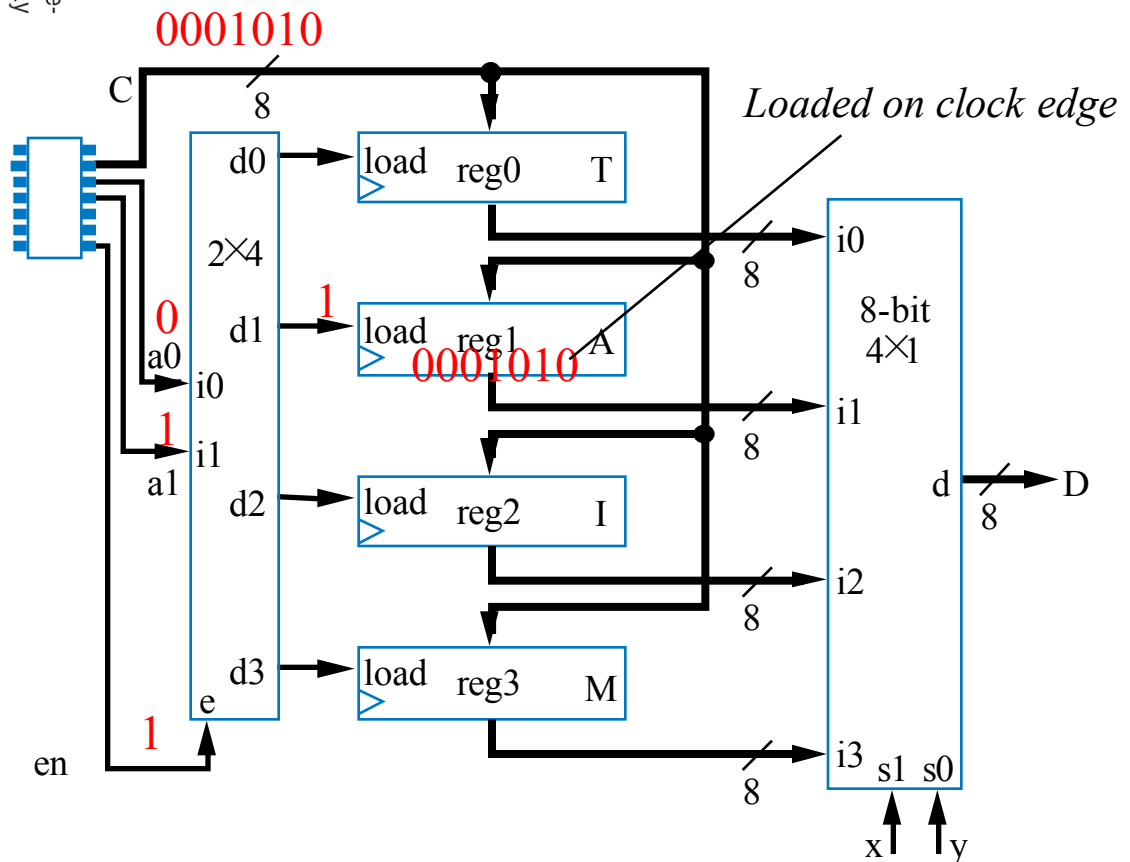- Four simultaneous values from car's computer: Temperature, Average mpg, Instantaneous mpg, Millage remaining
- To reduce wires: Computer writes only 1 value at a time, loads into one of four registers




Register Files

- ***MxN register file***


provides efficient
access to M N-bit-wide
registers

 - If we have many registers but only need access one or two at a time, a register file is more efficient
- Ex: Above mirror display (earlier example), but this time having 16 32-bit registers
 - Too many wires, and big mux is too slow



Register File

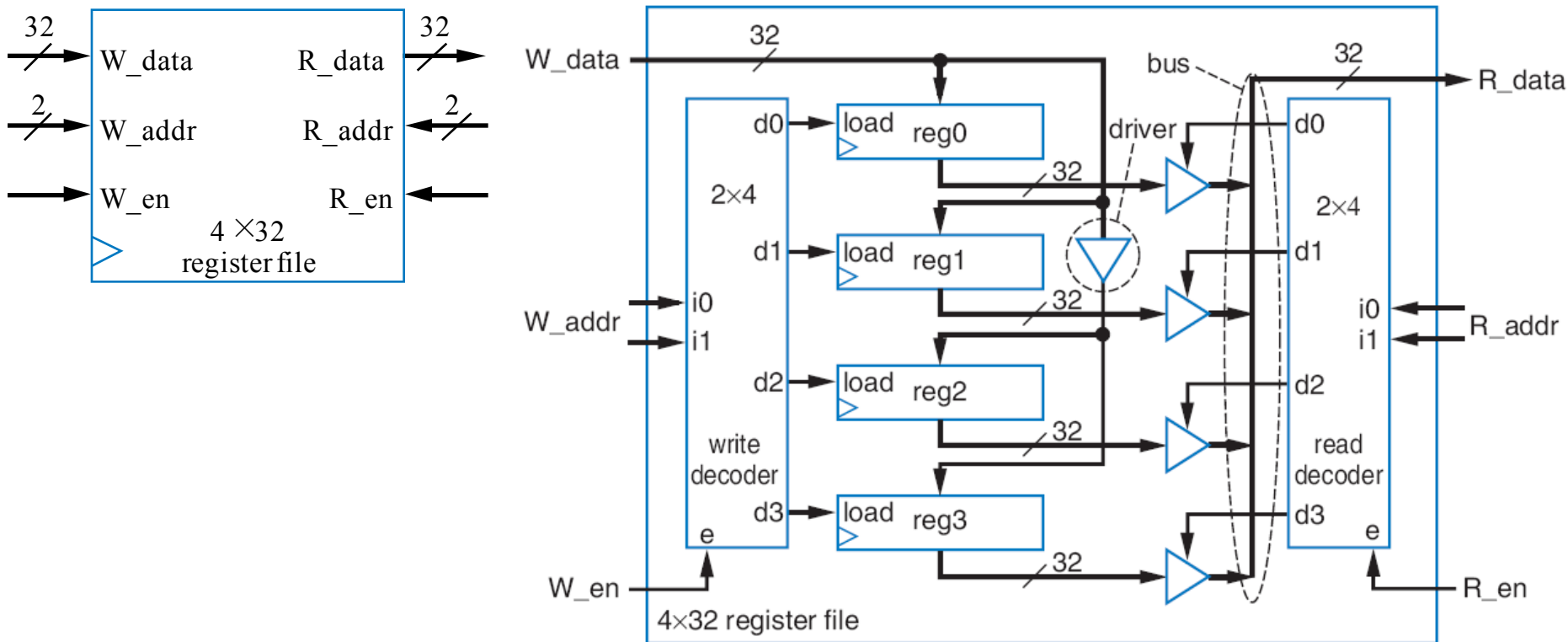- Instead, want component that has one data input and one data output, and allows us to specify which internal register to write and which to read





Verilog Modeling of Clocked Register File

```
module memory (R_data, W_data, W_addr, R_addr, W_en, R_en, clock);  
    parameter width = 32;  
    parameter addr_width = 2;  
    parameter number = 2**addr_width;  
  
    output [width-1:0]      R_data;  
    input  [width-1:0]      W_data;  
    input  [addr_width-1:0] W_addr, R_addr;  
    input                                W_en, R_en, clock;  
  
    reg [width-1:0] R_data;  
    reg [width-1:0] memory [number-1:0];  
  
    always @(posedge clock) begin  
        R_data = 'bz;  
        if (W_en)      memory[W_addr] = W_data;  
        else if (R_en) R_data = memory[R_addr]; //R_data will be register  
    end  
endmodule
```


Register File Timing Diagram

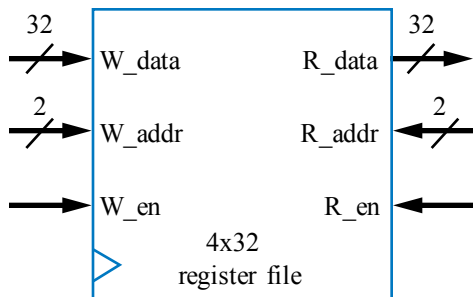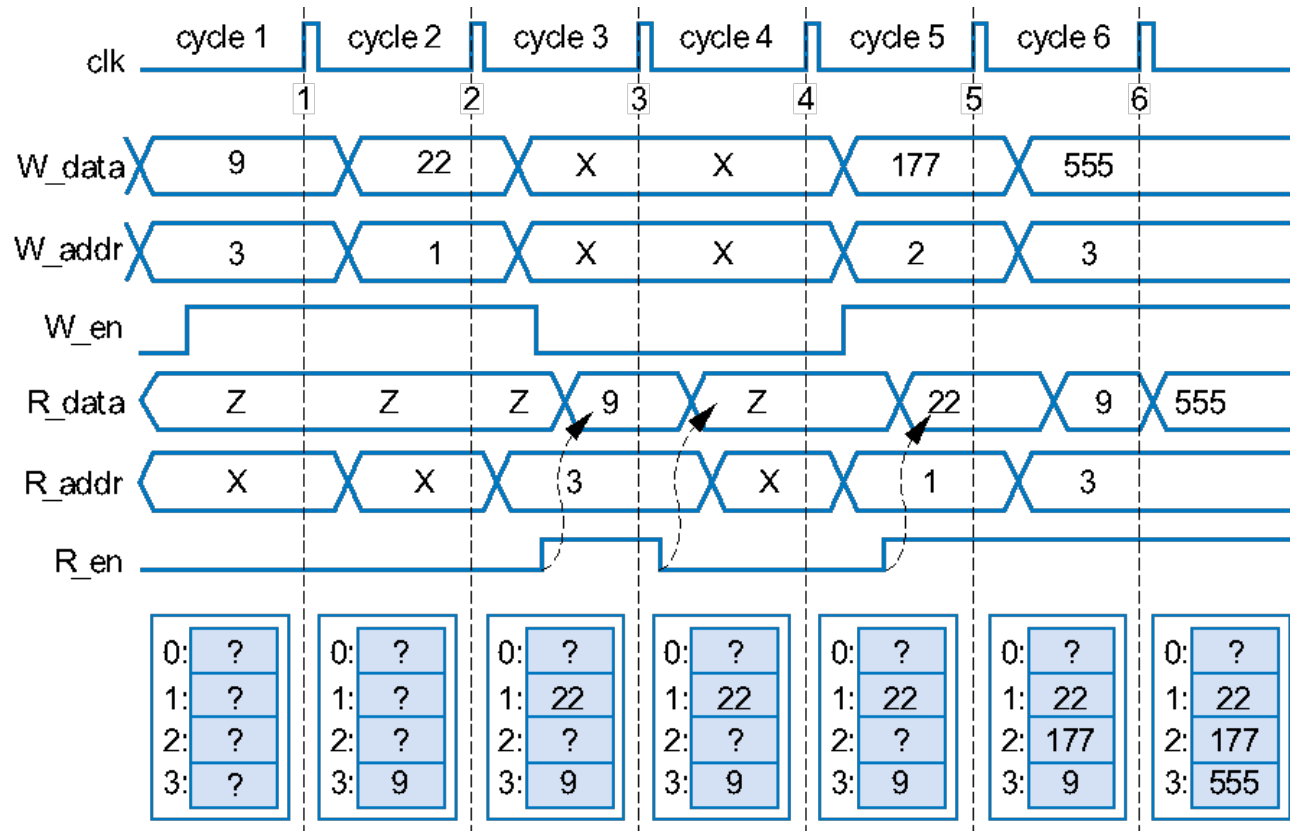- May be designed to write one register and read one register in one clock cycle
 - May be same register




Register-File Example: Above-Mirror Display

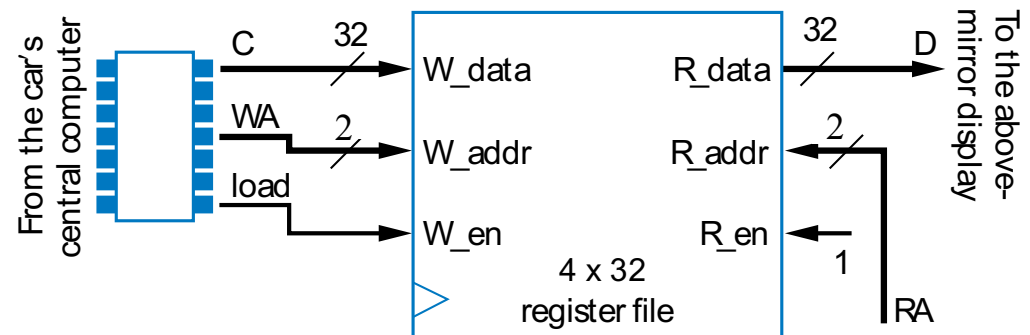- Four 32-bit registers that can be written by car's computer, and displayed
 - Use 4x32 register file
 - Simple, elegant design
- Register file hides complexity internally
 - And because only one register needs to be written and/or read at a time, internal design is simple




Shift Register

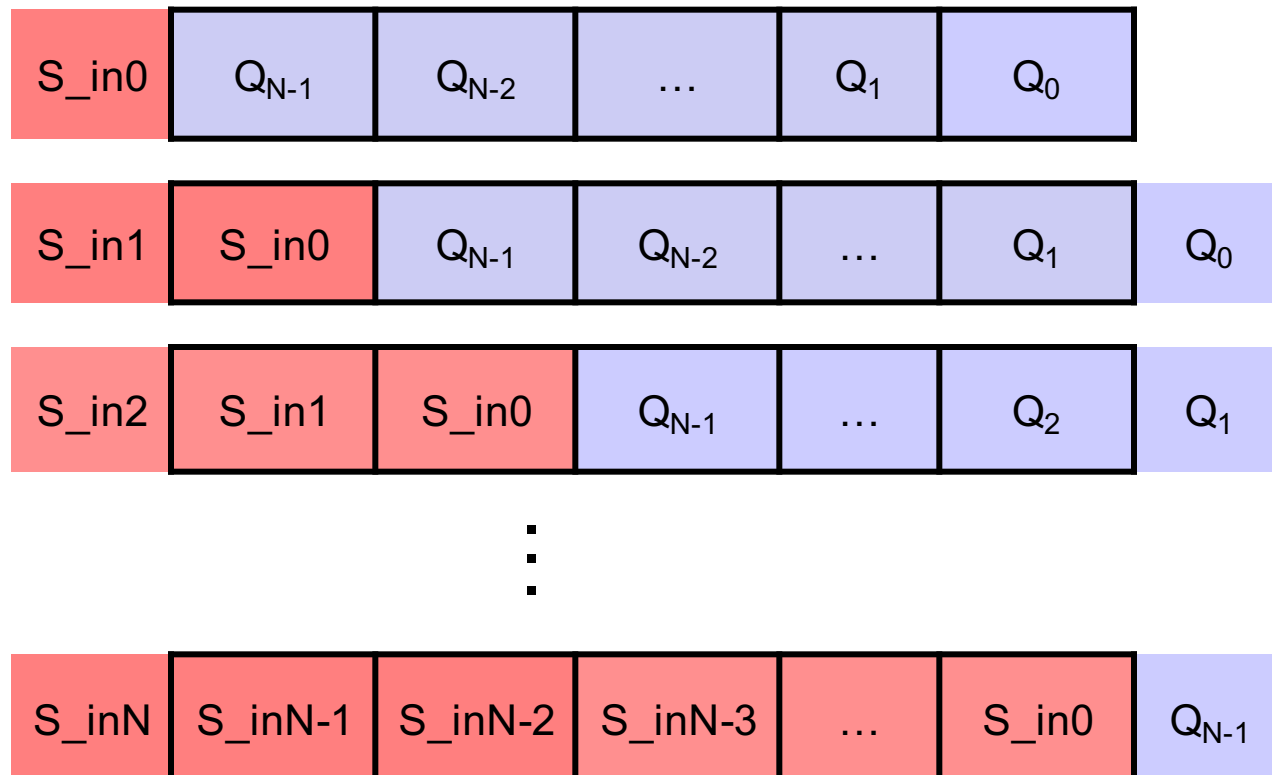- One type of register
 - Stores binary data
 - Stored data can be shifted right (MSB >> LSM) or left (MSB << LSB)
 - Example: Shift right per clock edge



Shift Register

 - Implementation:
 - Connect Q output of one flip flop to the D input of the next flip flop
 - 4-bit shift register



| | IN | OUT(3:0) |
|----------------|----|----------|
| Initial value: | 0 | 0110 |
| rising edge: | 0 | 0011 |
| rising edge: | 0 | 0001 |
| rising edge: | 0 | 0000 |
| rising edge: | 1 | 1000 |
| rising edge: | 0 | 0100 |

Verilog Modeling of Shift Registers

```
module Shift_Reg (Q, Dout, Din, clock);  
    input clock, Din;  
    output Dout;  
    output [3:0] Q;  
  
    reg [3:0] Q;  
  
    always @ (posedge clock)  
    begin  
        Q[2:0] <= Q[3:1];  
        Q[3]    <= Din;  
    end  
  
    assign Dout = Q[0];  
endmodule
```

Verilog Testbench for Shift Registers

```
module Test_Banch;
    parameter half_period = 50;
    wire [3:0] Q;  wire Dout;  reg  Din, clock;

    Shift_Reg UUT (Q, Dout, Din, clock);

    initial begin
        $display("*****");
        $display("The textual simulation results:");
        $display("*****");
        $monitor($time, "clock = %d  Din = %b  Q = %b  Dout = %d",
                clock, Din, Q, Dout);
    end

    initial begin
        #0    clock = 0; Din = 0;
        #300 Din = 1;
        #400 Din = 0;
    end

    always #half_period clock = ~clock;

    initial #1000 $stop;
endmodule
```


Textural Simulation Result

The textual simulation results:

| | | | | |
|-----|-----------|---------|----------|----------|
| 0 | clock = 0 | Din = 0 | Q = xxxx | Dout = x |
| 50 | clock = 1 | Din = 0 | Q = 0xxx | Dout = x |
| 100 | clock = 0 | Din = 0 | Q = 0xxx | Dout = x |
| 150 | clock = 1 | Din = 0 | Q = 00xx | Dout = x |
| 200 | clock = 0 | Din = 0 | Q = 00xx | Dout = x |
| 250 | clock = 1 | Din = 0 | Q = 000x | Dout = x |
| 300 | clock = 0 | Din = 1 | Q = 000x | Dout = x |
| 350 | clock = 1 | Din = 1 | Q = 1000 | Dout = 0 |
| 400 | clock = 0 | Din = 1 | Q = 1000 | Dout = 0 |
| 450 | clock = 1 | Din = 1 | Q = 1100 | Dout = 0 |
| 500 | clock = 0 | Din = 1 | Q = 1100 | Dout = 0 |
| 550 | clock = 1 | Din = 1 | Q = 1110 | Dout = 0 |
| 600 | clock = 0 | Din = 1 | Q = 1110 | Dout = 0 |
| 650 | clock = 1 | Din = 1 | Q = 1111 | Dout = 1 |
| 700 | clock = 0 | Din = 0 | Q = 1111 | Dout = 1 |
| 750 | clock = 1 | Din = 0 | Q = 0111 | Dout = 1 |
| 800 | clock = 0 | Din = 0 | Q = 0111 | Dout = 1 |
| 850 | clock = 1 | Din = 0 | Q = 0011 | Dout = 1 |
| 900 | clock = 0 | Din = 0 | Q = 0011 | Dout = 1 |
| 950 | clock = 1 | Din = 0 | Q = 0001 | Dout = 1 |


Stopped at time : 1.000 ps : File "C:/Users/gzheng/test/tb.v" Line 29

Graphical Simulation Results

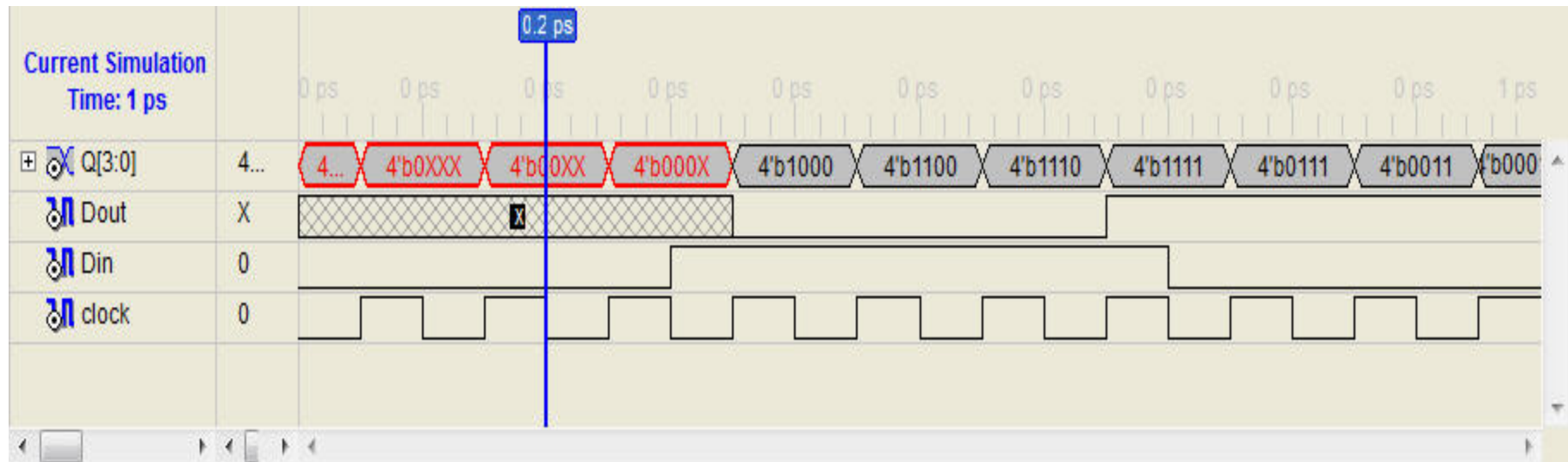

Rotate Register

 - Implementation:
 - Connect Q output of one flip flop to the D input of the next flip flop
 - Connect Q output of the last flip flop to the D input of the first flip flop
 - 4-bit rotate register



| | OUT(3:0) |
|----------------|----------|
| Initial value: | 0110 |
| rising edge: | 0011 |
| rising edge: | 1001 |
| rising edge: | 1100 |
| rising edge: | 0110 |
| rising edge: | 0011 |

Verilog Modeling of Rotate Registers


```
module Barral_Shift_Reg (Q, clock);  
    input clock;  
    output [3:0] Q;  
  
    reg [3:0] Q;  
  
    always @ (posedge clock)  
    begin  
        Q[2:0] <= Q[3:1];  
        Q[3] <= Q[0];  
    end  
  
endmodule
```

Modified Rotate Registers

```
module Barral_Shift_Reg (Q, Din, clock, ld);  
  input clock, ld, Din;  
  output [3:0] Q;  
  
  reg [3:0] Q;  
  
  always @ (posedge clock)  
  begin  
    Q[2:0] <= Q[3:1];  
    if (ld) Q[3] <= Din;  
    else    Q[3] <= Q[0];  
  end  
  
endmodule
```



Shift/Rotate Register with Control Input

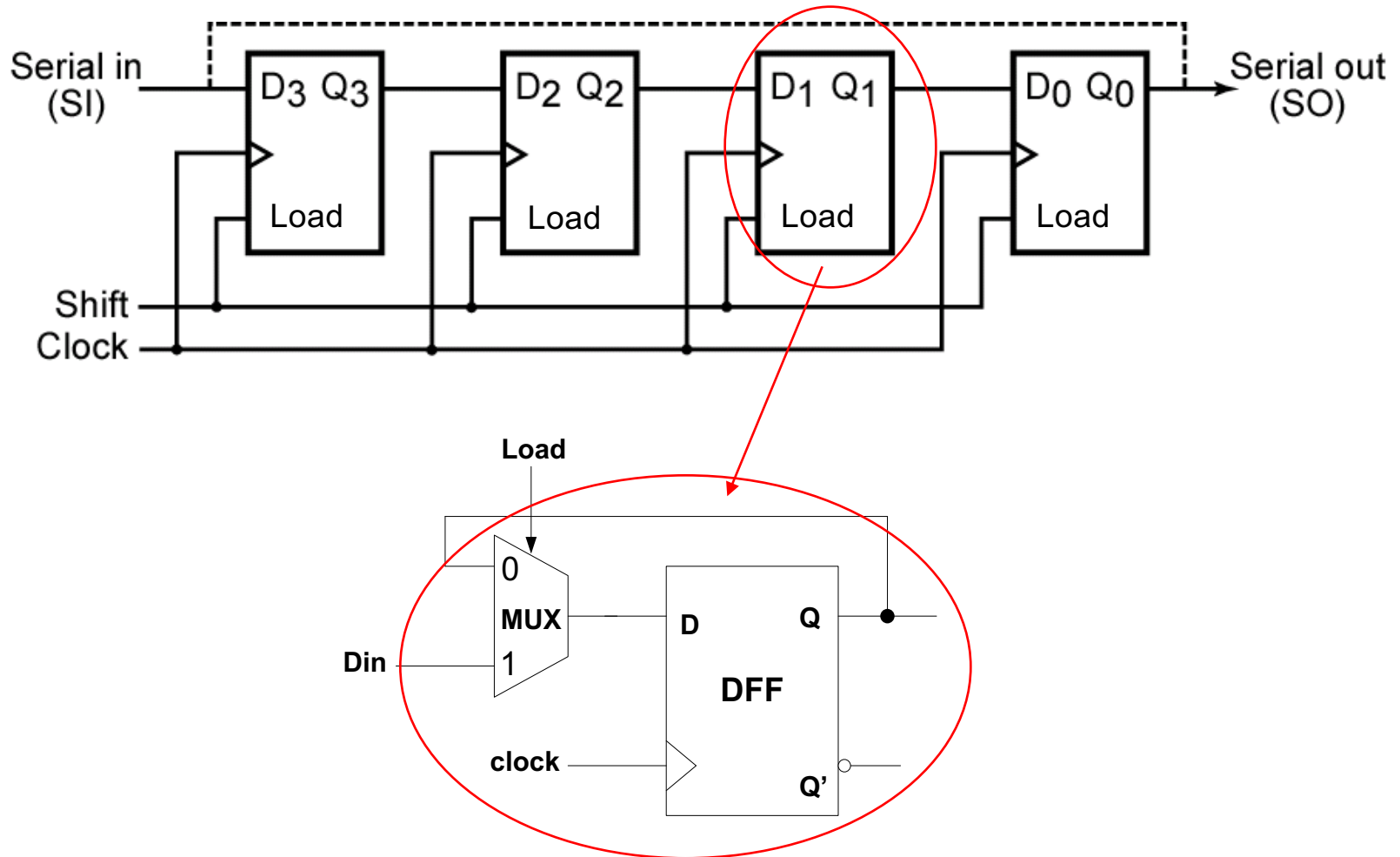 - Parallel Load control input may be used to hold the shifting



Universal Shift Register

- Multi-functional shift register





- Functions
 - the 4th input of MUX can be used for something else


| Inputs | | Action |
|------------|----------|-------------|
| Sh (Shift) | L (Load) | |
| 0 | 0 | no change |
| 0 | 1 | load |
| 1 | X | Shift Right |

Shift Register Example: Above-Mirror Display

  
- Earlier example: $8 + 2 + 1 = 11$ wires from computer to registers
- Use shift registers
 - Wires: $1 + 2 + 1 = 4$
 - Computer sends one value at a time, one bit per clock cycle



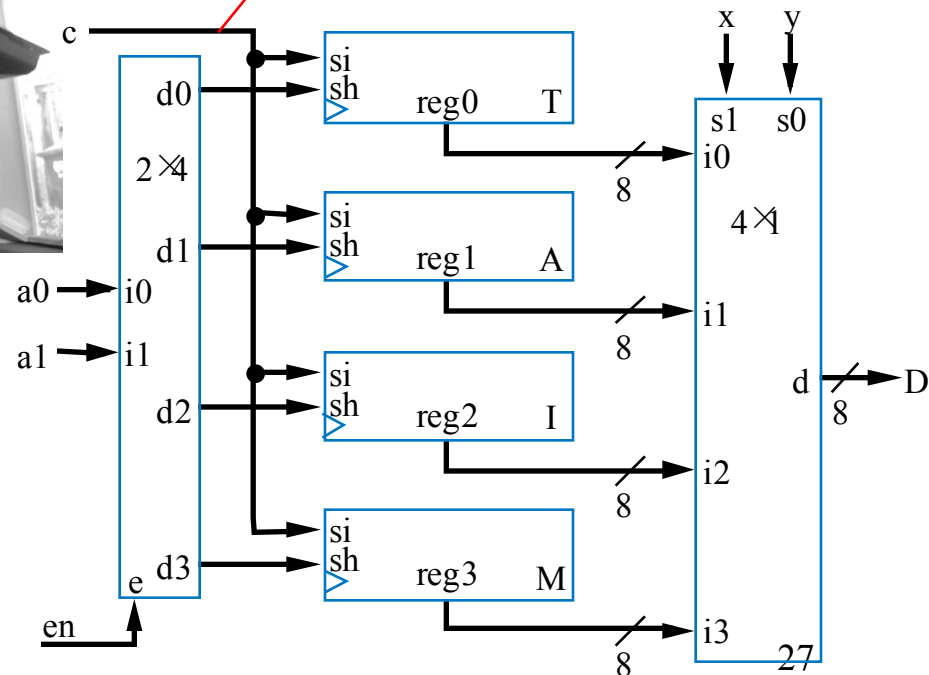Note: this line is 1 bit, rather than 8 bits like before




The diagram illustrates the USART hardware architecture. At the top, the **Internal Data Bus** (32 bits wide) connects to the **Transmit FIFO** (up to 8 levels deep) via **Write** operations. The FIFO is divided into **TX8 FIFO Slot⁽¹⁾** (bits 32-9) and **TX4 FIFO Slot⁽²⁾** (bits 8-0). Data from the FIFO is loaded into the **Transmit Shift Register (UxTSR)**. The **Transmit Control** block manages the UxTSR, buffer, flags, and interrupts. It is connected to **UxMODE** and **UxSTA** registers. The **Transmit Shift Register (UxTSR)** outputs **Data**, **(Start)**, **(Stop)**, and **Parity** signals to a multiplexer. The **Parity Generator** and **Divider** blocks receive **Control Signals** and the **Baud Clock from Baud Rate Generator**. The **UTXBRK** signal is also shown.

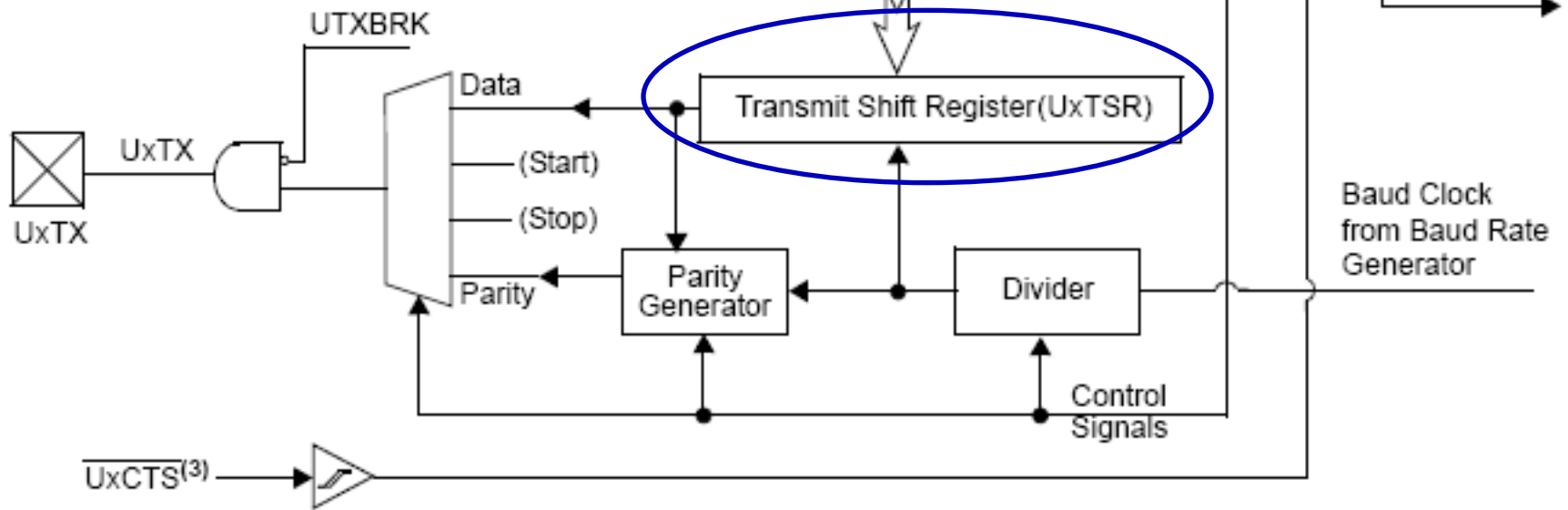

Shifters (Not Shift Register)

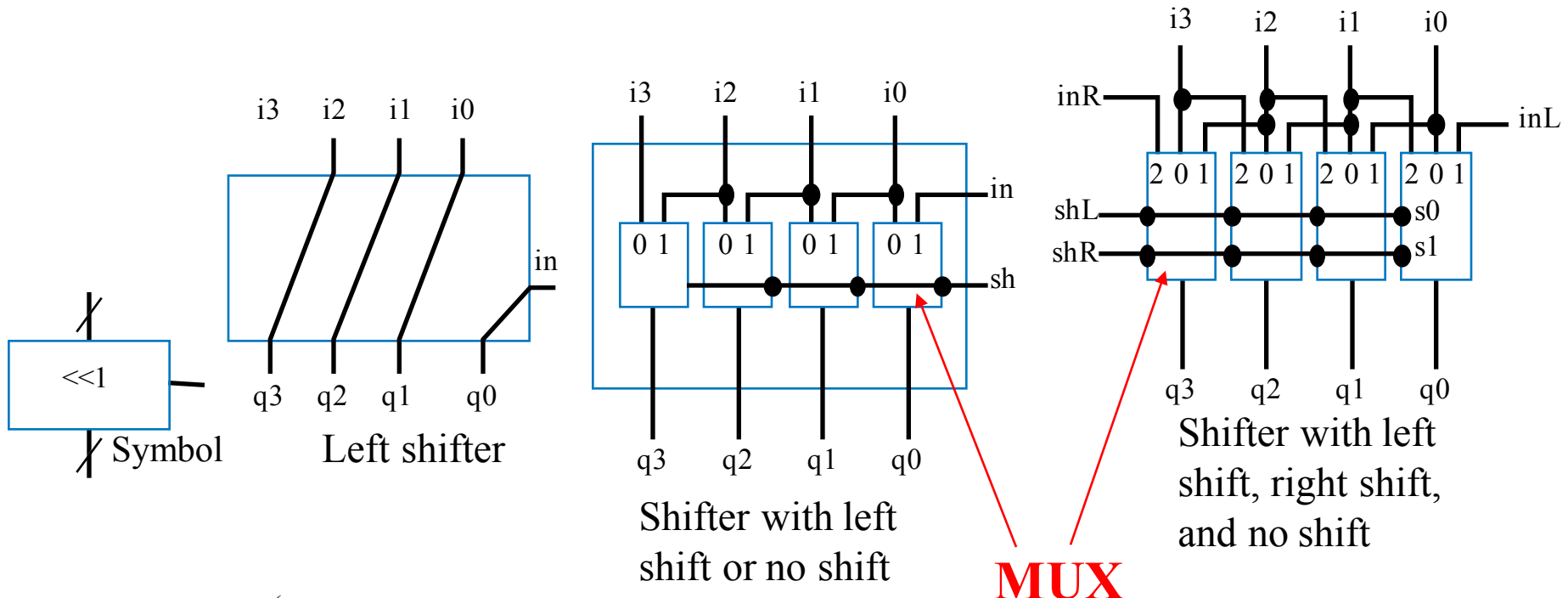- Combinational Datapath component
- Shifting (e.g., left shifting 0011 yields 0110) useful for:
 - Manipulating bits
 - Shift left once is same as multiplying by 2 (0011 (3) becomes 0110 (6))
 - Shift right once same as dividing by 2



Verilog Modeling of Shifter

```
module Shifter_0_or_1 (Q, I, in, sh);
    parameter size = 4;
    input in, sh;
    input [size-1:0] I;
    output [size-1:0] Q;


    reg [size-1:0] Q;

    always @ (sh, in, I)
    begin
        if (sh) begin Q[size-1:1] = I[size-2:0];
                    Q[0]          = in;
                end
        else Q = I;
    end

endmodule
```


Shifter Example: Approximate Celsius to Fahrenheit Converter

 - Convert 8-bit Celsius input to 8-bit Fahrenheit output
 - $F = C * 9/5 + 32$
 - Approximate: $F = C * 2 + 32$
 - Use left shift: $F = \text{left_shift}(C) + 32$



Shifter Example: Temperature Averager

 - Four registers storing a history of temperatures
- Want to output the average of those temperatures
- Add, then divide by four
 - Same as shift right by 2
 - Use three adders, and right shift by two



Bigger Shifter

- A shifter that can shift by any amount
 - But shifting too many bits in one shifter could require design with too many wires
- More elegant design
 - Chain shifters
 - E.g.: Can achieve any shift of 0..7 bits by enabling the correct combination of 4, 2, 1 bit shifters

