



JOINT INSTITUTE  
交大密西根学院

---

Ve 270 Introduction to Logic Design

# **Lab 6**

## **Design of a Keypad Reader**

UM-SJTU Joint Institute  
Shanghai Jiao Tong University  
November 2017


### 1. Objective

To design a Finite State Machine that reads the keys from a 4-by-4 keypad and displays the corresponding hexadecimal value on an SSD.

### 2. Background

Keypad readers are used to interpret data entered from keypads for digital devices such as phones, calculators, digital lock, etc. A keypad reader decodes a pressed key and outputs the corresponding binary code. Figure 1 shows the connection between a hexadecimal keypad and the keypad reader circuit.

When a button is pressed, it connects a row and a column at the location of the button. By providing a 1 to a column of the keypad, a 1 will be received from the connected row. In other words, the pressed key creates a loop for the signal 1 to travel from the keypad reader, through the loop created by the pressed key, and back to the keypad reader.

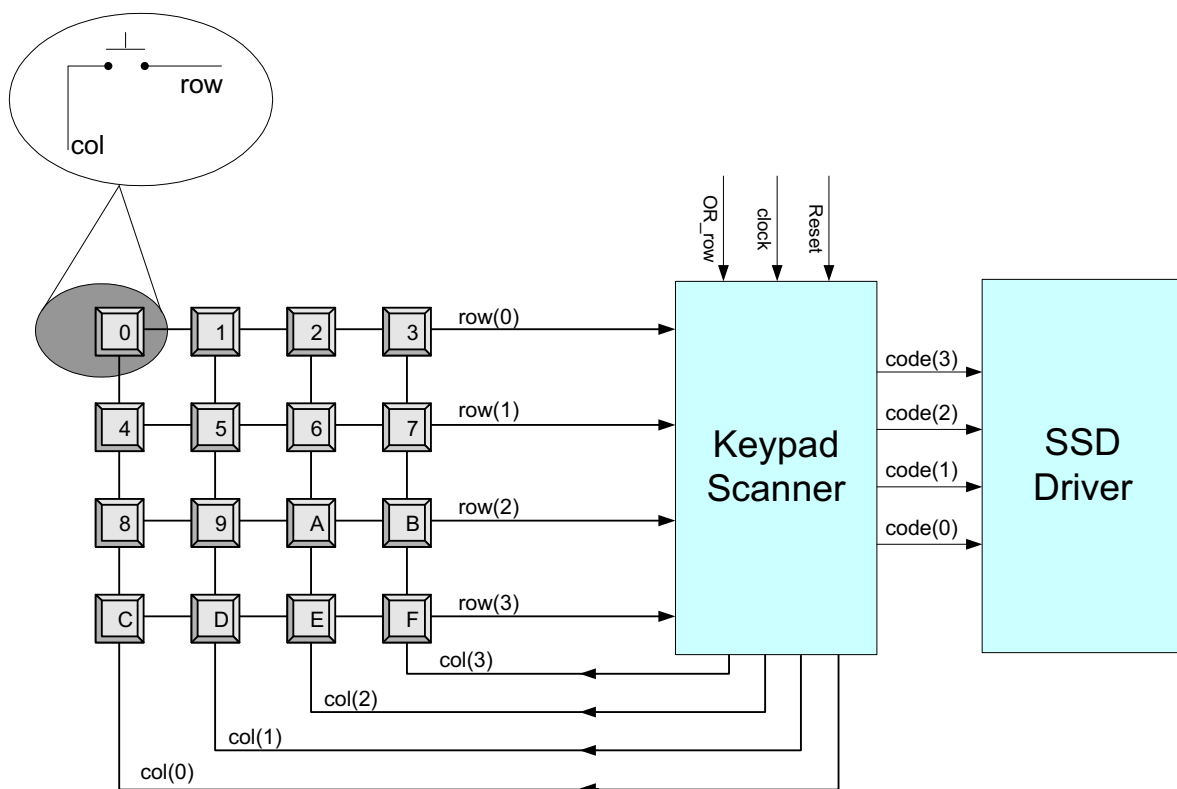

**Figure 1. Keypad Reader**

The keypad reader must be able to fire a column line to detect the location of a pressed button. A keypad reader detects a pressed key in three steps:


- (1) Detects whether a key is pressed;
- (2) Identifies which key is pressed;
- (3) Generates the corresponding 4-bit hexadecimal code for the pressed key.

Step (1) can be achieved by outputting “1111” on the *col* output, so that one of the *row* inputs will be asserted whenever there is a key pressed. An OR logic of all the *row* inputs (*OR\_row*) will be used to indicate whether any row is high. If the keypad reader detects a high on the *OR\_row* output, it performs step (2) in which the *col* outputs will be turned on sequentially. This will tell which row and column are connected. Thus, the pressed key can be located. Step (3) will be done by looking it up in Table 1.

**Table 1. Keypad code for the Hex keypad**

Key	row (3 : 0)	col (3 : 0)	code (3 : 0)
0	0001	0001	0000
1	0001	0010	0001
2	0001	0100	0010
3	0001	1000	0011
4	0010	0001	0100
5	0010	0010	0101
6	0010	0100	0110
7	0010	1000	0111
8	0100	0001	1000
9	0100	0010	1001
A	0100	0100	1010
B	0100	1000	1011
C	1000	0001	1100
D	1000	0010	1101
E	1000	0100	1110
F	1000	1000	1111

This keypad reader can be designed as a Finite State Machine. The key detecting algorithm is captured in Figure 2. The machine begins in State0, with all of the *col* outputs asserted, until one of the *row* inputs is asserted. From State1 to State4, only one of the *col* outputs is asserted. If one of the *row* inputs is also asserted, the pressed key is located. An output code can be determined by the combination of *col* outputs and *row* inputs. The FSM then moves to State5 where it outputs the *code* with all the *col* outputs asserted until the *OR\_row* is de-asserted which indicates the key is released.

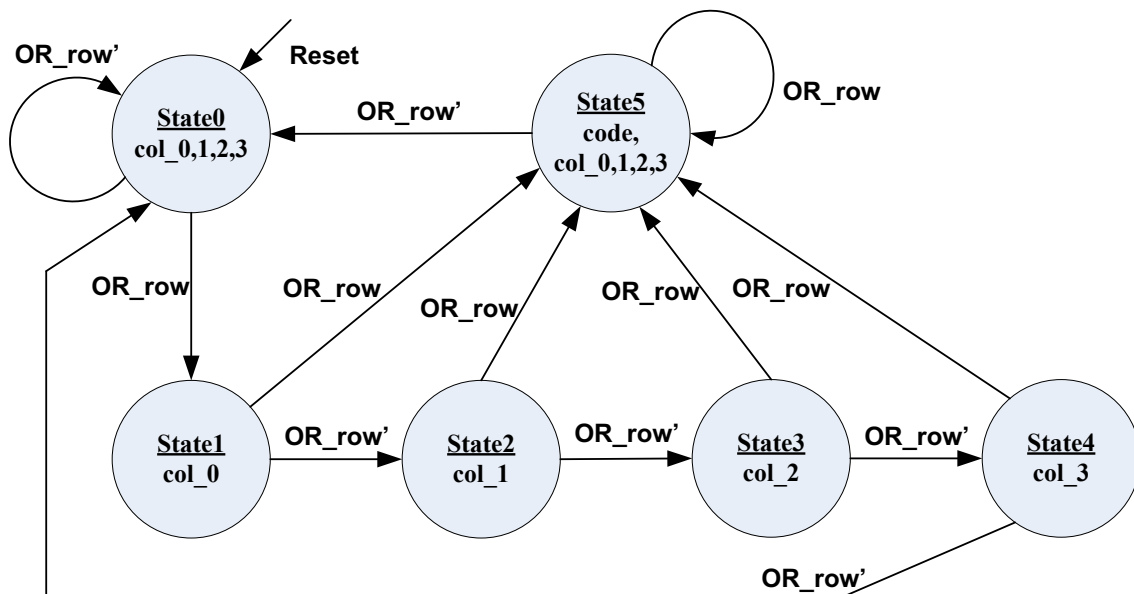

**Figure 2. State diagram of the keypad reader**



**Note: use a 1 Hz clock to trigger the state machine, and use LEDs on the board to display the current state of the FSM.**

### 3. Verilog Coding

Write a Verilog module for the Keypad Reader as an FSM following the state diagram shown in Figure 2. The FSM should have an asynchronous reset. Connect the SSD Driver developed in Lab 3 to display the interpreted hexadecimal value.

### 4. Simulation, Synthesis, and FPGA Implementation

Simulate the top-level integrated circuit using HDL Benchner. Synthesize and implement your design on the Basys 3 FPGA board.

### 5. Deliverable

This is a 2-week lab. The full score for this lab is 200 points.

- 1) Demonstrate your circuits to the TAs before your lab session ends.
- 2) Upload source files on Canvas by **10pm, November 24, 2017**.
- 3) Upload peer evaluation report on Canvas by **10pm, November 24, 2017**.

Peer evaluation form:

Name	Percentage of contribution (sum to 100%)	Responsibilities
(yourself)		
(your lab partner)		