


Topic 2

Basic Logic Gates

Electronic Switch – Transistors


- **Transistors are the basis of binary digital circuits**

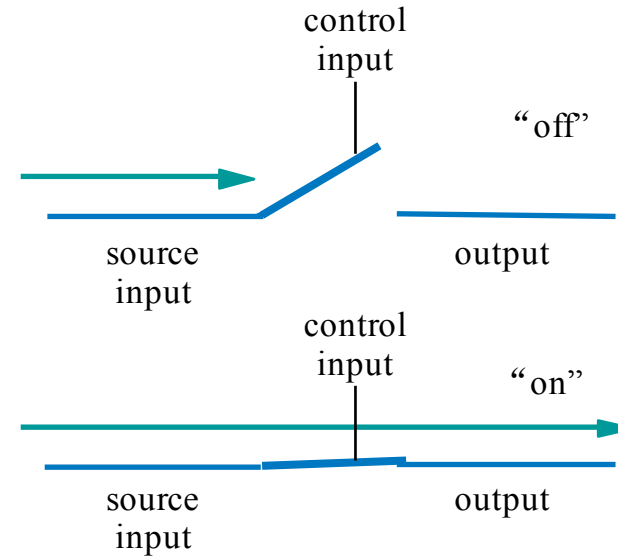- Transistors operate at 2 values
H / L or
On / Off or
1 / 0




- **Evolution of electronic switches**

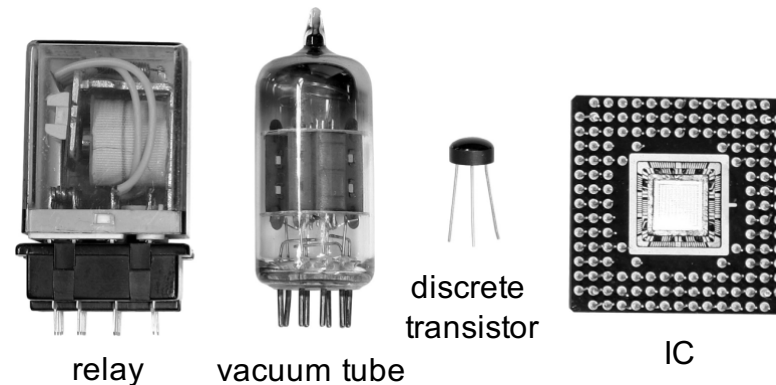- 1930s: Relays
- 1940s: Vacuum tubes
- 1950s: Discrete transistor
- 1960s: Integrated circuits (ICs)
 - Initially just a few transistors on IC
 - Then tens, thousands, millions...



Moore's Law


- **IC capacity doubling about every 18 months for several decades**
 - Known as “Moore’s Law” after Gordon Moore, co-founder of Intel
 - Predicted in 1965 predicted that components per IC would double roughly every 18 months or so
 - For a particular number of transistors, the IC shrinks by half every 18 months
 - Enables incredibly powerful computation in incredibly tiny devices
 - Today’s ICs hold *billions* of transistors
 - The first Pentium processor (early 1990s) had only 3 million

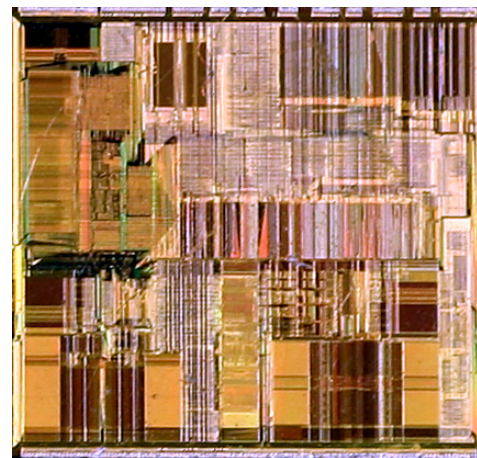


An Intel Pentium processor IC having millions of transistors

CMOS Transistor

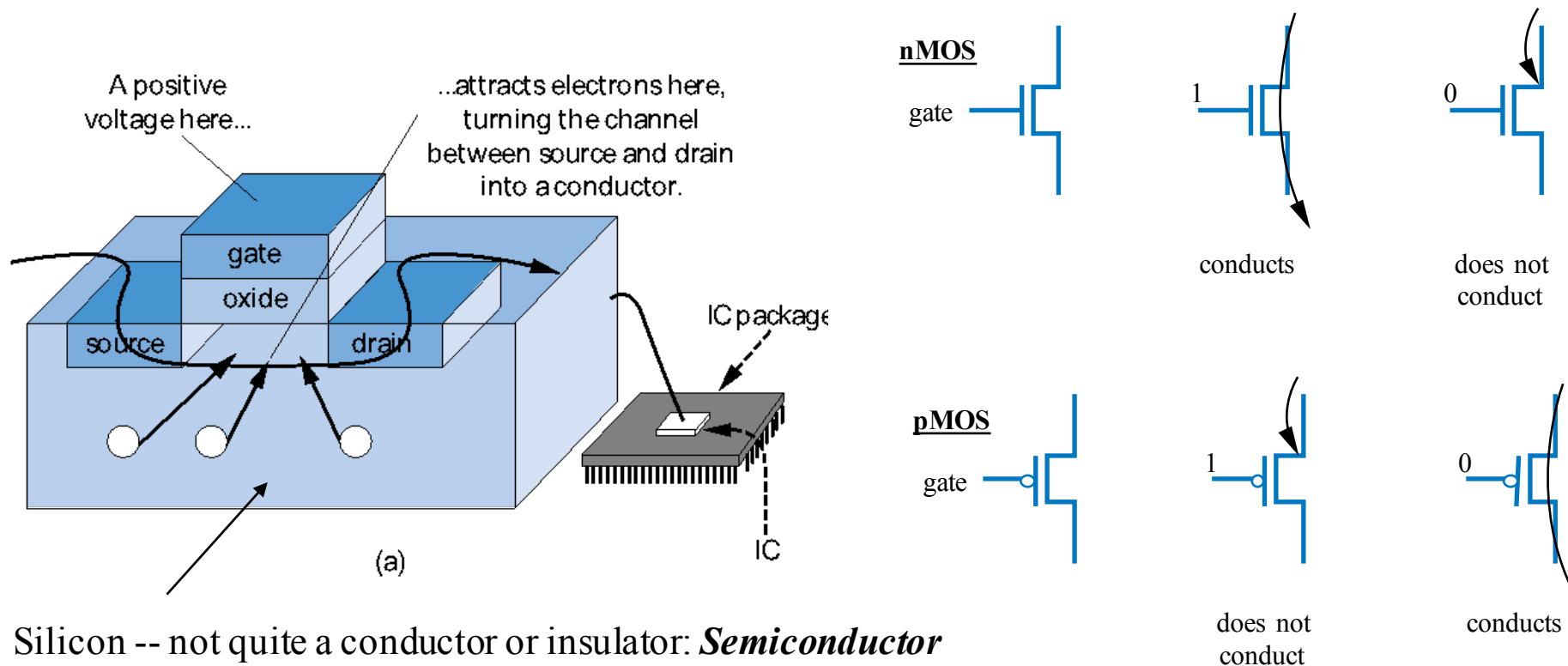- **CMOS – Complementary Metal-Oxide-Semiconductor**
- **Transistors with CMOS technology**



AND Logic


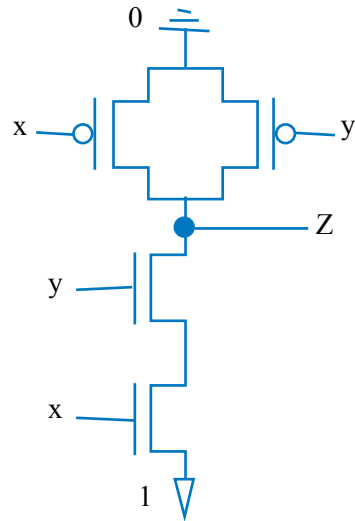


X	Y	Z = XY
0	0	0
0	1	0
1	0	0
1	1	1

Truth Table

- Definition of AND operation**

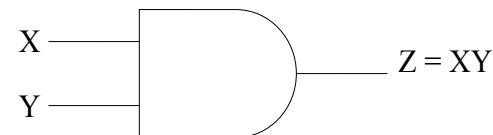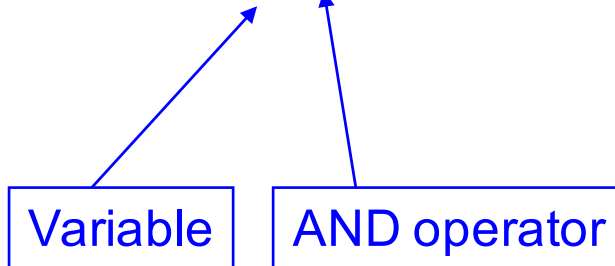$Z = X \cdot Y$ means $Z = 1$ if and only if both $X = 1$ and $Y = 1$;




2-input AND gate

Truth Table

- **Truth table creates the relationship between the inputs and outputs**

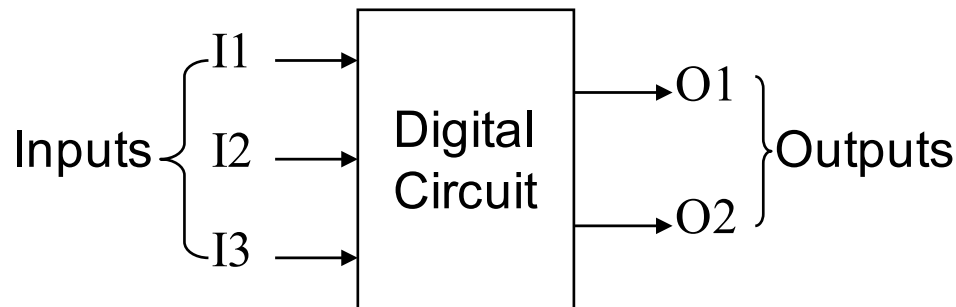- Must include all the inputs to the device in the left columns
- Must include all the outputs of the device in the right columns
- The behavior of the circuit is implied by the table



Number of combinations is 2^N ; N is the number of the inputs

Inputs			Outputs	
I1	I2	I3	O1	O2
0	0	0	?	?
0	0	1	?	?
0	1	0	?	?
0	1	1	?	?
1	0	0	?	?
1	0	1	?	?
1	1	0	?	?
1	1	1	?	?

Example of Truth Table

a	b	F
0	0	
0	1	
1	0	
1	1	

(a)


a	b	c	F
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

(b)

a	b	c	d	F
0	0	0	0	
0	0	0	1	
0	0	1	0	
0	0	1	1	
0	1	0	0	
0	1	0	1	
0	1	1	0	
0	1	1	1	
1	0	0	0	
1	0	0	1	
1	0	1	0	
1	0	1	1	
1	1	0	0	
1	1	0	1	
1	1	1	0	
1	1	1	1	

(c)

OR Logic

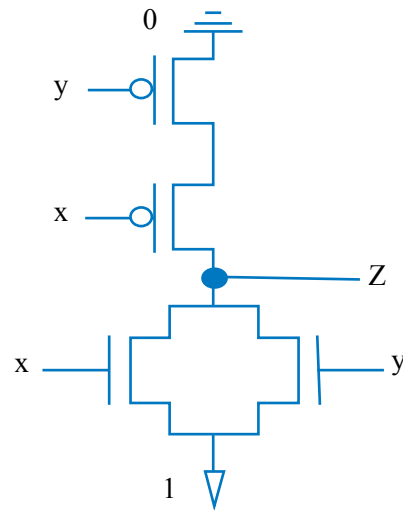


X	Y	Z = X + Y
0	0	0
0	1	1
1	0	1
1	1	1

Truth Table

- Definition of OR operation**


$Z = X + Y$ means $Z = 1$ if either $X=1$ or $Y=1$, or both;

OR operator

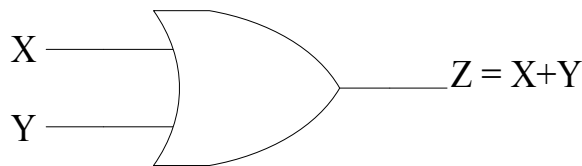

2-input OR gate

NOT Logic

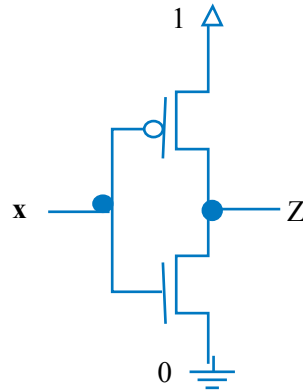


X	Z = X'
0	1
1	0

Truth Table

- Definition of NOT operation**


$Z = X'$ or $Z = \overline{X}$ means $Z = 0$ if $X = 1$; $Z = 1$ if $X = 0$; Z is the complement of X

NOT operator

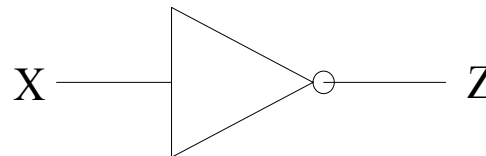


NOT gate/Inverter

Logic Gates

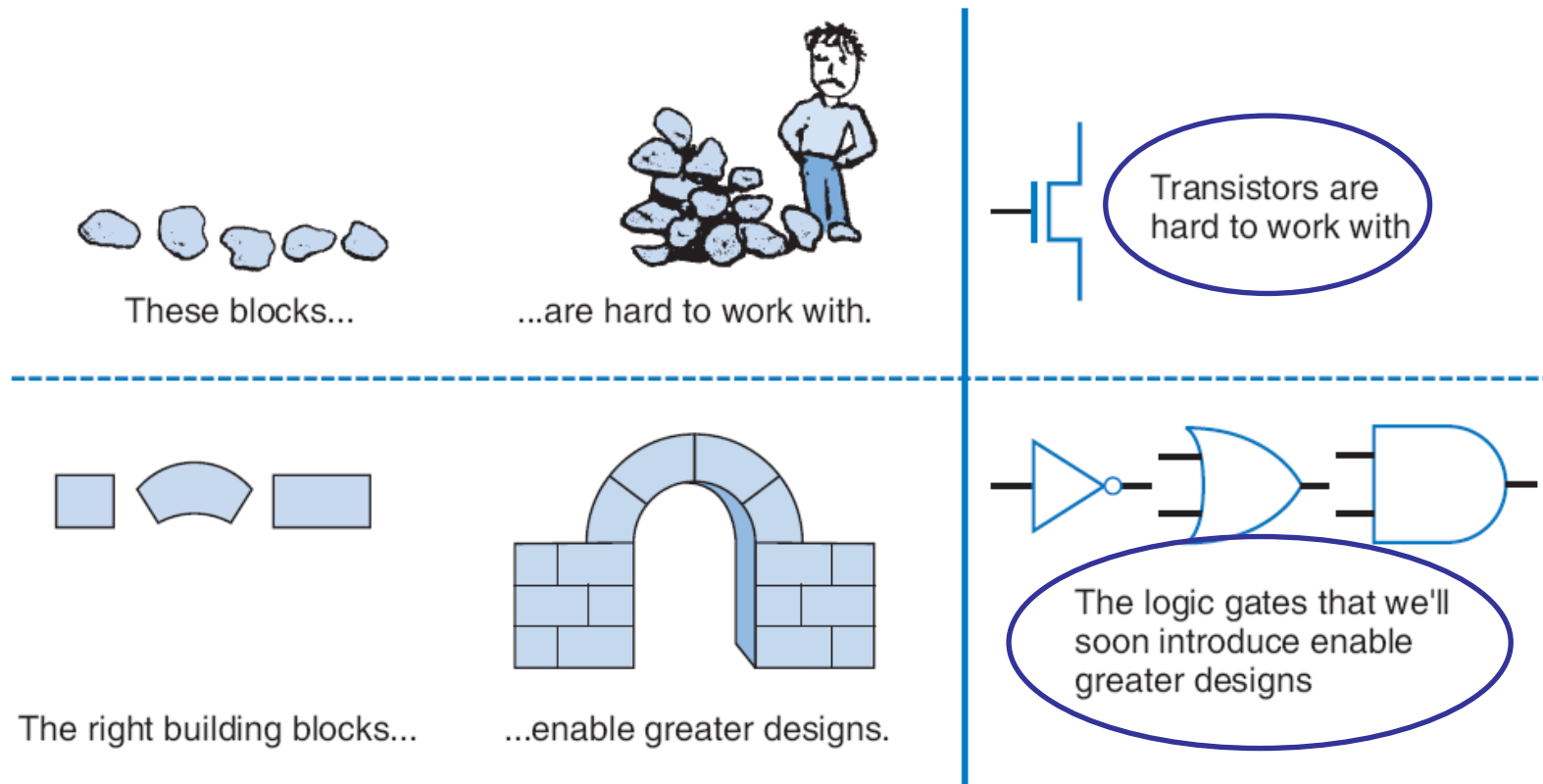

- **“Logic gates” are better digital circuit building blocks than switches (transistors)**

Logics in Human Language

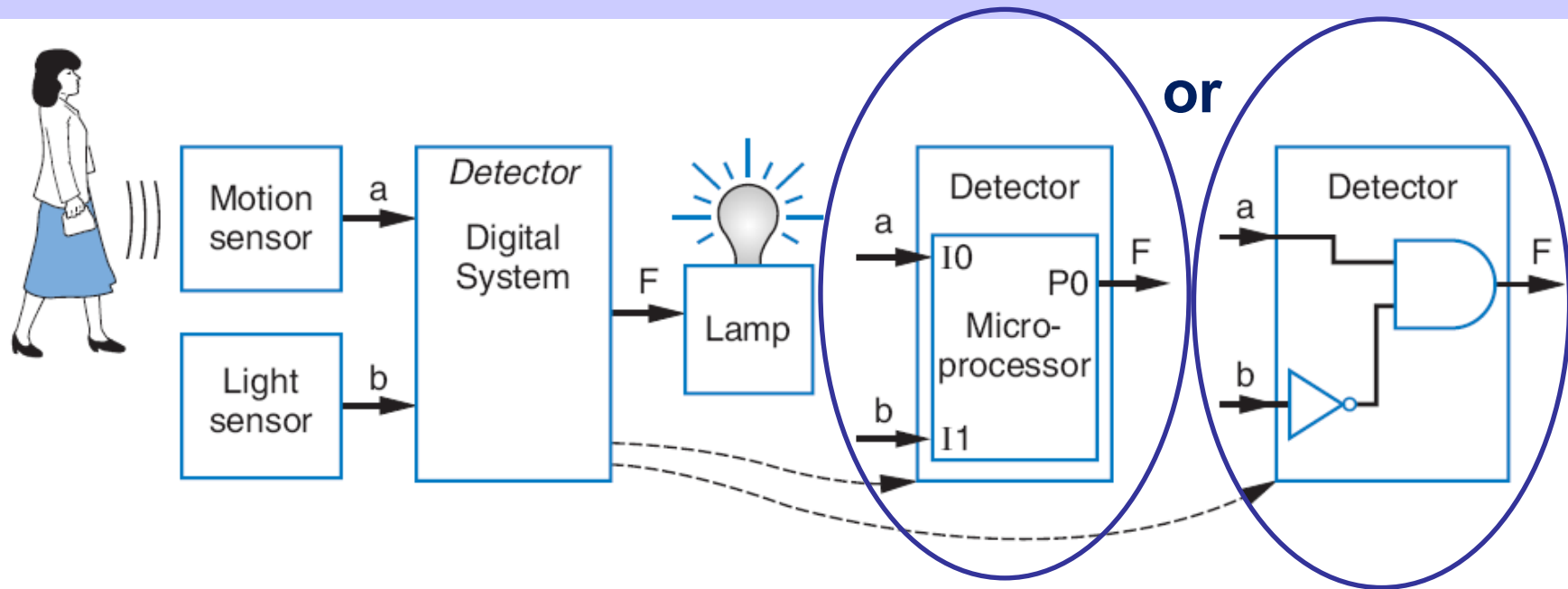


- **Motion-in-dark example**

- Human language: Turn on lamp ($F=1$) when motion sensed (a) and no light (not b)
- *Logic Equation*: $F = a \text{ AND NOT}(b) = ab'$
- *Logic circuit*: implementation using logic gates, AND and NOT, as shown

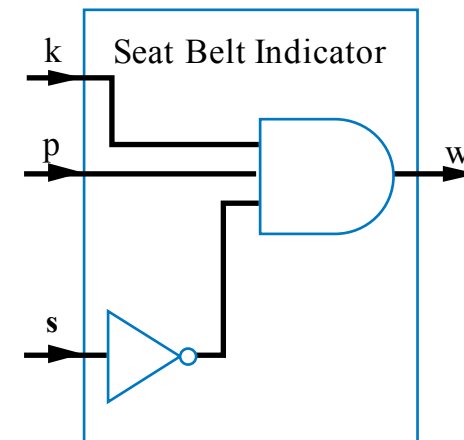Example: Seat Belt Warning Light System


- **Design circuit for warning light**
- **Sensors**
 - $s=1$: seat belt fastened
 - $k=1$: key inserted
 - $p=1$: person in seat
- **Function description**
 - Light on if person in seat, and seat belt not fastened, and key inserted
- **Logic equation**
$$w = p \text{ AND } \text{NOT}(s) \text{ AND } k$$



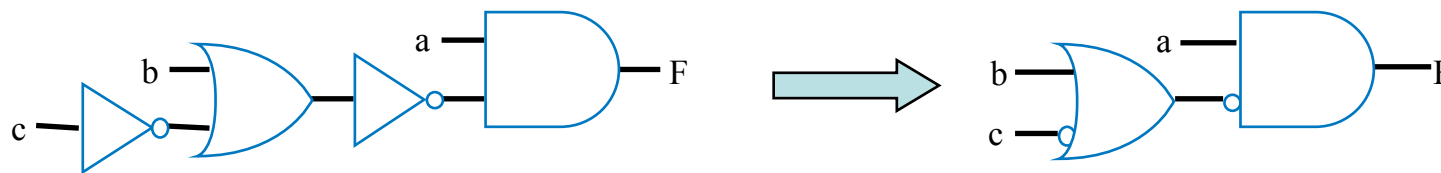Example: Represent Logic Equation with Logic Gates

- Q: Convert the following equation to logic gates:


$$F = a \text{ AND NOT}(b \text{ OR NOT}(c))$$



- Precedence of Logic Operations
NOT > AND > OR

From Logic Equation to Logic Circuit

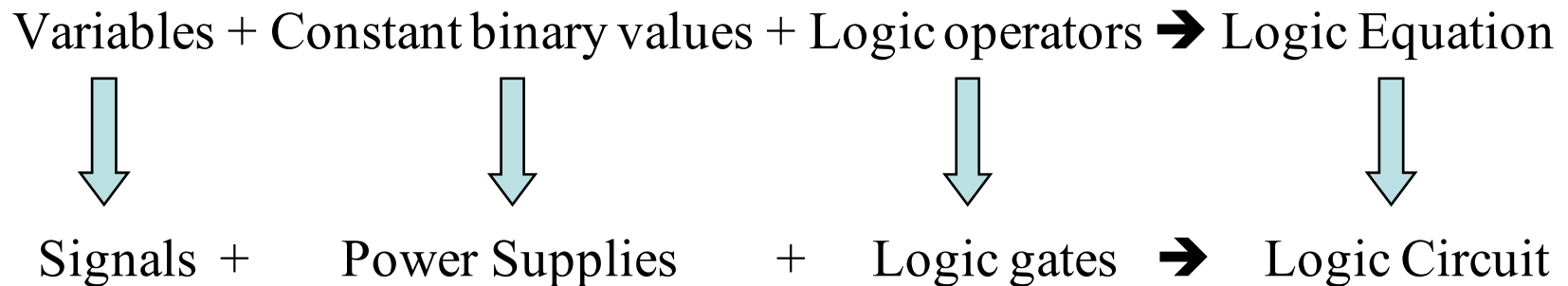- There exists a correspondence between a Logic Equation and its logic circuit.






- **Logic Circuit:**
A net of logic gates.

Logic Equation and Logic Circuit


- **$F = x \text{ OR } (\text{NOT } y \text{ AND } z)$**

$$= x + y'z$$

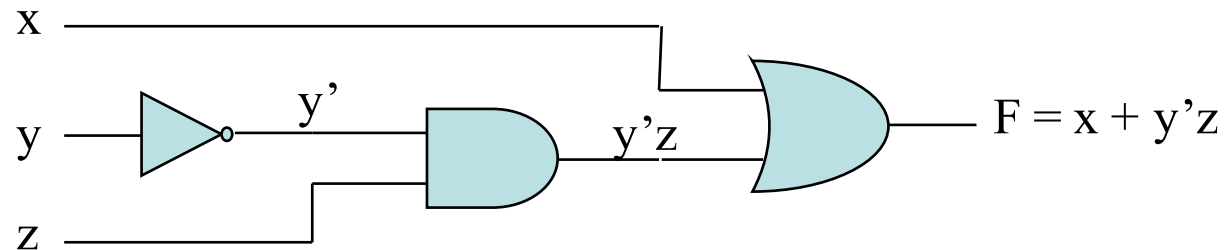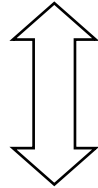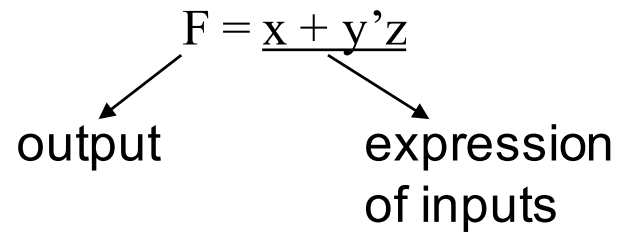

Build Truth Table

- $F = x + y'z$

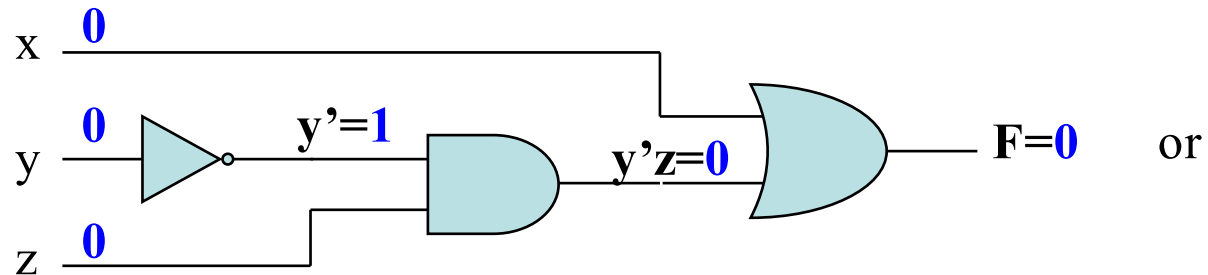


$$\begin{aligned}
 F &= 0 + 0' \cdot 0 \\
 &= 0 + 1 \cdot 0 \\
 &= 0 + 0 \\
 &= 0
 \end{aligned}$$

- Truth table

x	y	z	y'	y'z	F
0	0	0	1	0	0
0	0	1	?	?	?
0	1	0	?	?	?
0	1	1	?	?	?
1	0	0	?	?	?
1	0	1	?	?	?
1	1	0	?	?	?
1	1	1	?	?	?

Build Truth Table

- $F = x + y'z$

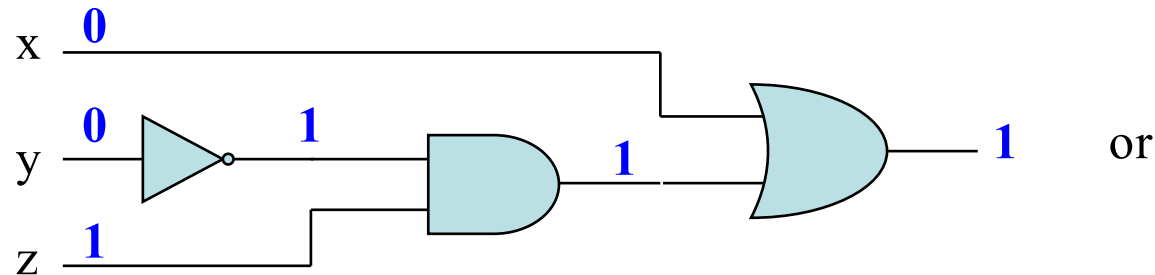


$$\begin{aligned} F &= 0 + 0' \cdot 1 \\ &= 0 + 1 \cdot 1 \\ &= 0 + 1 \\ &= 1 \end{aligned}$$

- Truth table

x	y	z	y'	$y'z$	F
0	0	0	1	0	0
0	0	1	1	1	1
0	1	0	?	?	?
0	1	1	?	?	?
1	0	0	?	?	?
1	0	1	?	?	?
1	1	0	?	?	?
1	1	1	?	?	?

Build Truth Table

- $F = x + y'z$

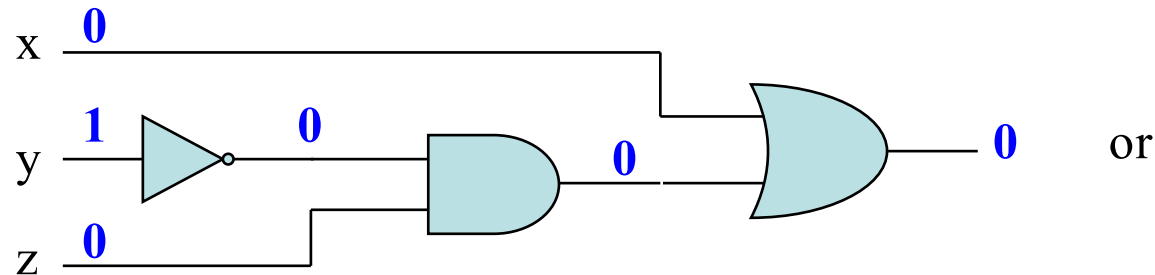


$$\begin{aligned} F &= 0 + 1' \cdot 0 \\ &= 0 + 0 \cdot 0 \\ &= 0 + 0 \\ &= 0 \end{aligned}$$

- Truth table

x	y	z	y'	$y'z$	F
0	0	0	1	0	0
0	0	1	1	1	1
0	1	0	0	0	0
0	1	1	?	?	?
1	0	0	?	?	?
1	0	1	?	?	?
1	1	0	?	?	?
1	1	1	?	?	?

Build Truth Table

- $F = x + y'z$

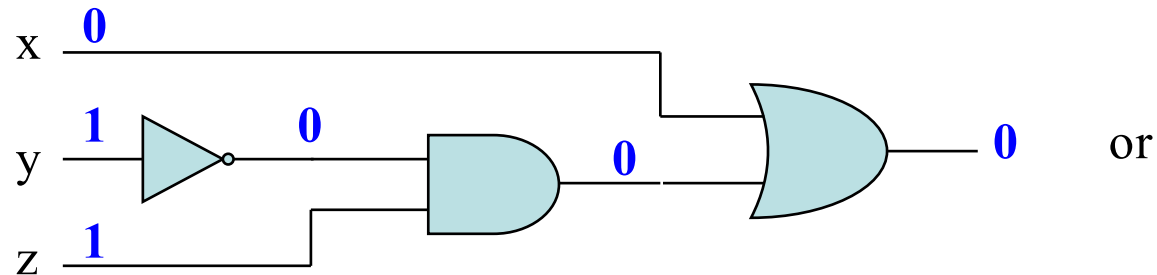


$$\begin{aligned} F &= 0 + 1' \cdot 1 \\ &= 0 + 0 \cdot 1 \\ &= 0 + 0 \\ &= 0 \end{aligned}$$

- Truth table

x	y	z	y'	$y'z$	F
0	0	0	1	0	0
0	0	1	1	1	1
0	1	0	0	0	0
0	1	1	0	0	0
1	0	0	?	?	?
1	0	1	?	?	?
1	1	0	?	?	?
1	1	1	?	?	?

Build Truth Table

- $F = x + y'z$

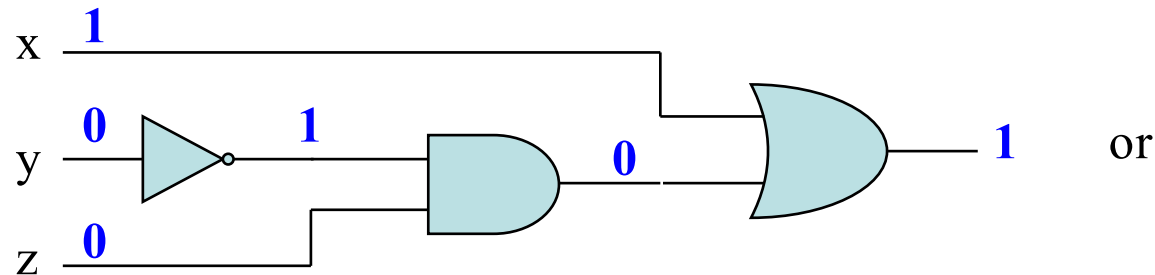


$$\begin{aligned} F &= 1 + 0' \cdot 0 \\ &= 1 + 1 \cdot 0 \\ &= 1 + 0 \\ &= 1 \end{aligned}$$

- Truth table

x	y	z	y'	$y'z$	F
0	0	0	1	0	0
0	0	1	1	1	1
0	1	0	0	0	0
0	1	1	0	0	0
1	0	0	1	0	1
1	0	1	?	?	?
1	1	0	?	?	?
1	1	1	?	?	?

Build Truth Table

- $F = x + y'z$

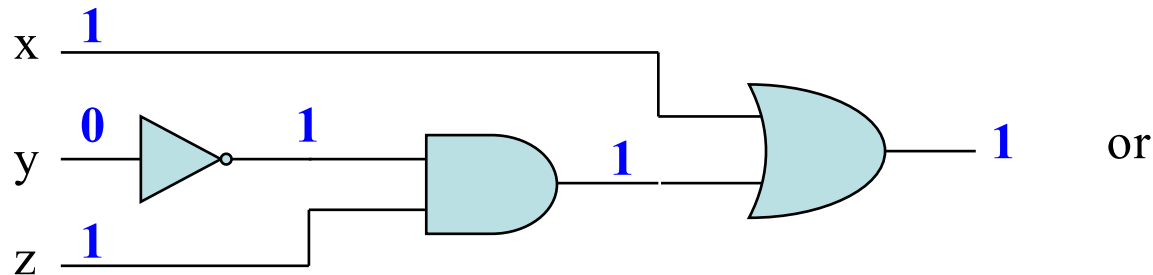


$$\begin{aligned} F &= 1 + 0' \cdot 1 \\ &= 1 + 1 \cdot 1 \\ &= 1 + 1 \\ &= 1 \end{aligned}$$

- Truth table

x	y	z	y'	y'z	F
0	0	0	1	0	0
0	0	1	1	1	1
0	1	0	0	0	0
0	1	1	0	0	0
1	0	0	1	0	1
1	0	1	1	1	1
1	1	0	?	?	?
1	1	1	?	?	?

Build Truth Table

- $F = x + y'z$

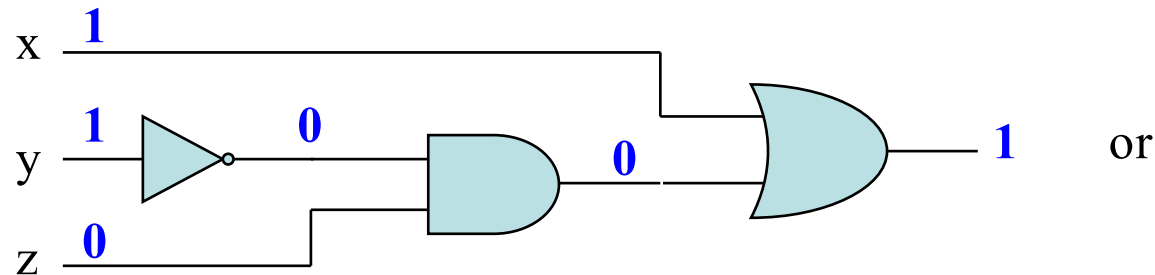


$$\begin{aligned}
 F &= 1 + 1' \cdot 0 \\
 &= 1 + 0 \cdot 0 \\
 &= 1 + 0 \\
 &= 1
 \end{aligned}$$

- Truth table

x	y	z	y'	y'z	F
0	0	0	1	0	0
0	0	1	1	1	1
0	1	0	0	0	0
0	1	1	0	0	0
1	0	0	1	0	1
1	0	1	1	1	1
1	1	0	0	0	1
1	1	1	?	?	?

Build Truth Table

- $F = x + y'z$

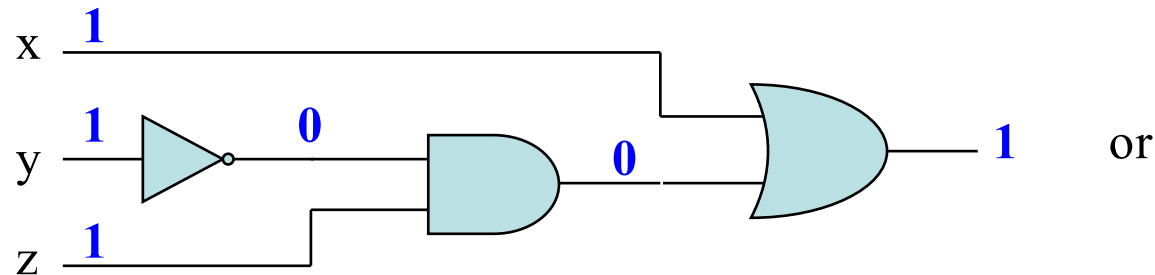


$$\begin{aligned} F &= 1 + 1' \cdot 1 \\ &= 1 + 0 \cdot 1 \\ &= 1 + 0 \\ &= 1 \end{aligned}$$

- Truth table

x	y	z	y'	y'z	F
0	0	0	1	0	0
0	0	1	1	1	1
0	1	0	0	0	0
0	1	1	0	0	0
1	0	0	1	0	1
1	0	1	1	1	1
1	1	0	0	0	1
1	1	1	0	0	1

Logic Equation, Truth Table, & Logic Circuit

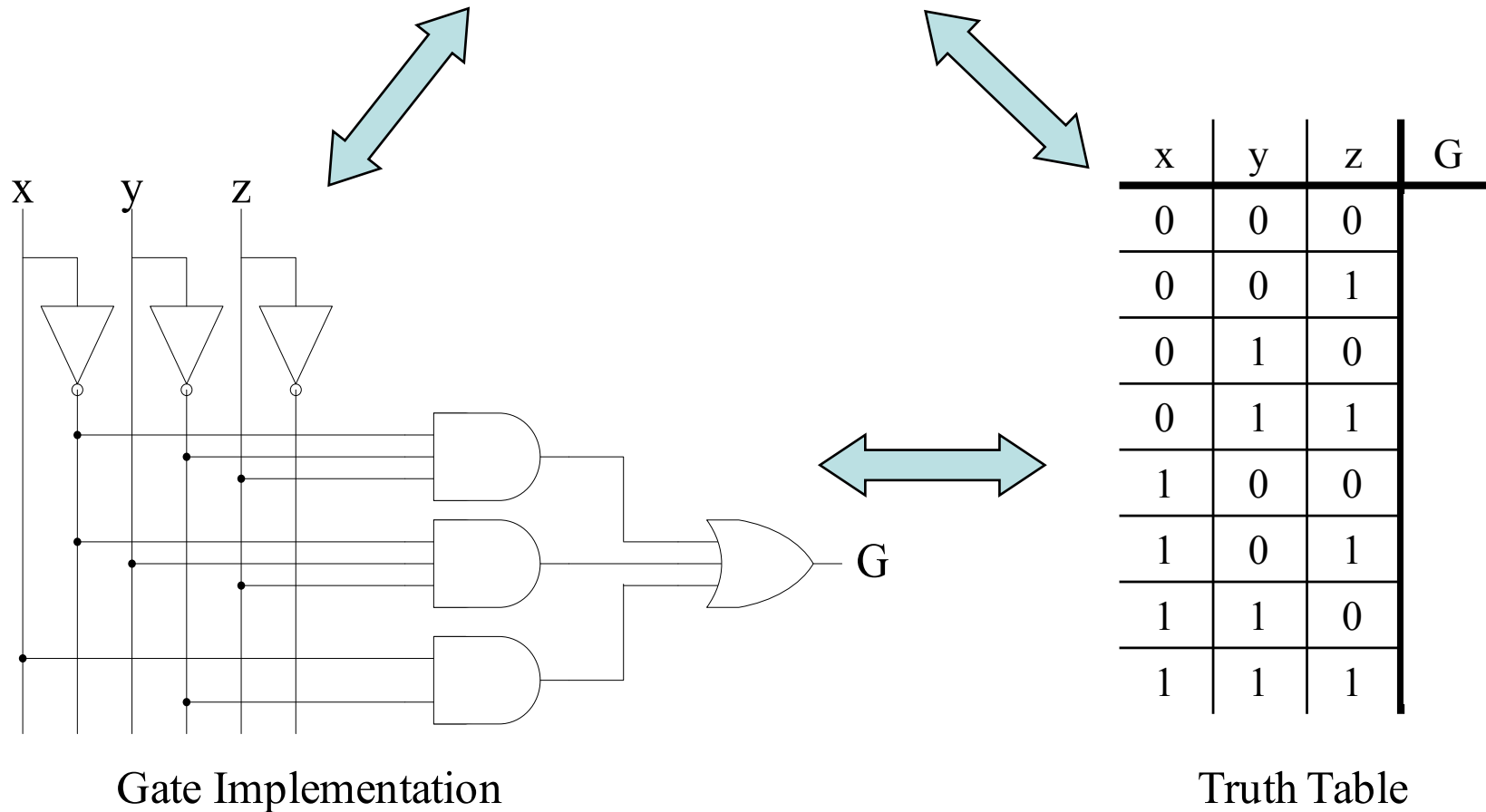- Another example: $G = x'y'z + x'yz + xy'$



Create Truth Table

a	b	F
0	0	
0	1	
1	0	
1	1	

(a)

a	b	c	F
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

(b)

a	b	c	d	F
0	0	0	0	
0	0	0	1	
0	0	1	0	
0	0	1	1	
0	1	0	0	
0	1	0	1	
0	1	1	0	
0	1	1	1	
1	0	0	0	
1	0	0	1	
1	0	1	0	
1	0	1	1	
1	1	0	0	
1	1	0	1	
1	1	1	0	
1	1	1	1	


(c)

- **Q: Use truth table to define function $F(a,b,c)$ that is 1 only when abc is 5 or greater in binary**

a	b	c	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

Timing Diagram

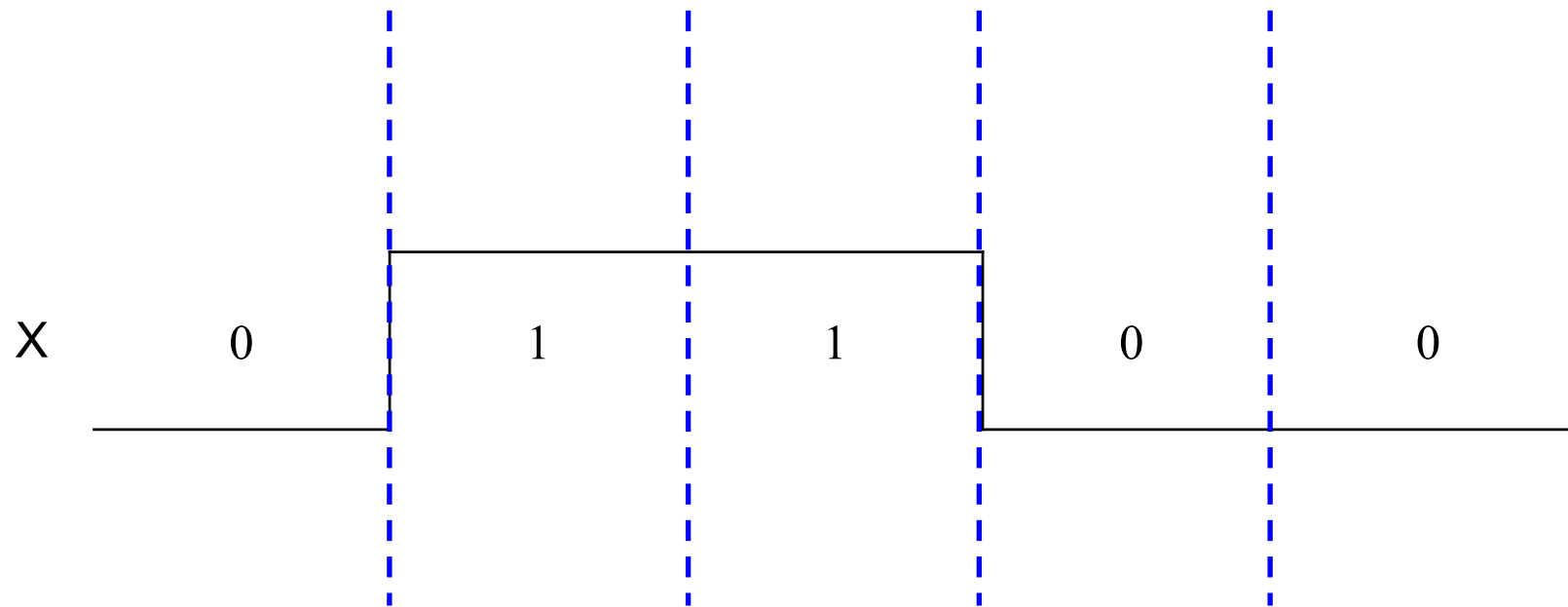- **Timing diagrams show the response to changes on a signal in voltage levels with time**




Timing Diagrams for Gates


xy	F
0 0	0
0 1	0
1 0	0
1 1	1

x+y	F
0 0	0
0 1	1
1 0	1
1 1	1


x	F
0	1
1	0

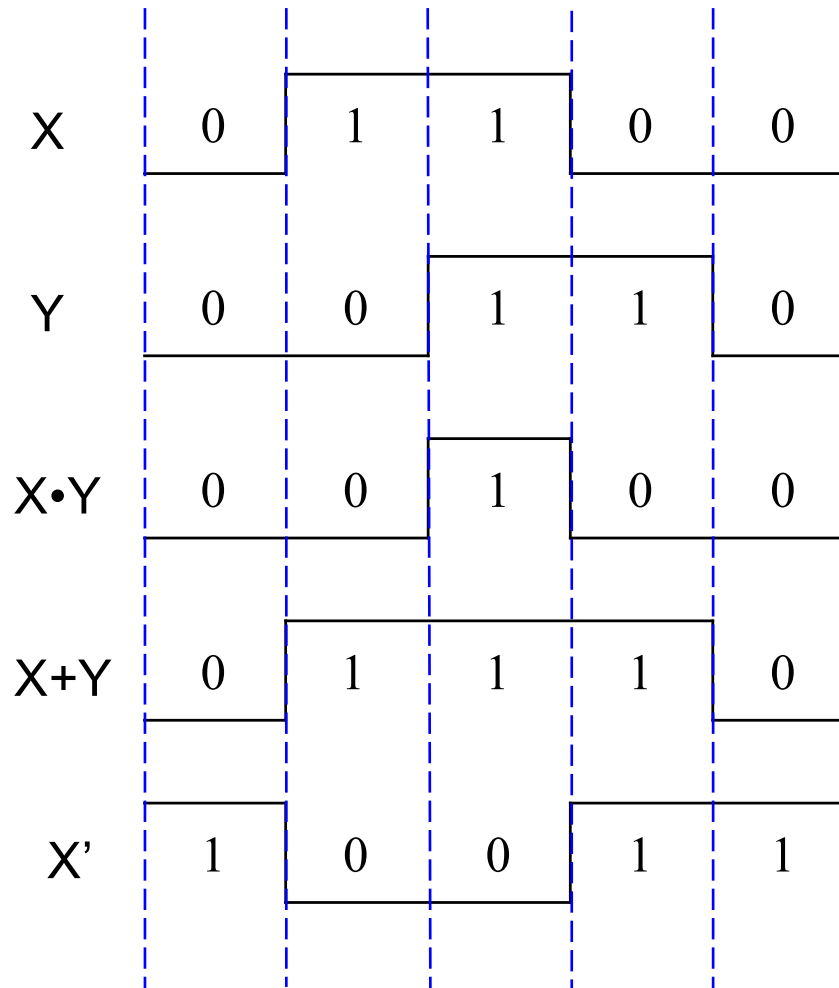


More Gates

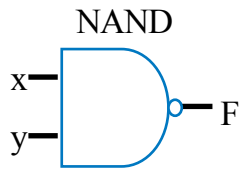


x	y	F
0	0	1
0	1	1
1	0	1
1	1	0

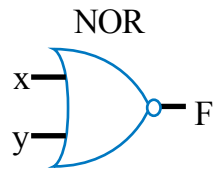

x	y	F
0	0	1
0	1	0
1	0	0
1	1	0


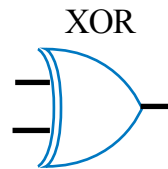


x	y	F
0	0	0
0	1	1
1	0	1
1	1	0

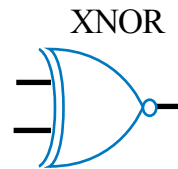

x	y	F
0	0	1
0	1	0
1	0	0
1	1	1

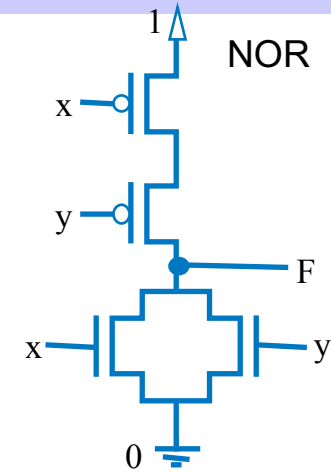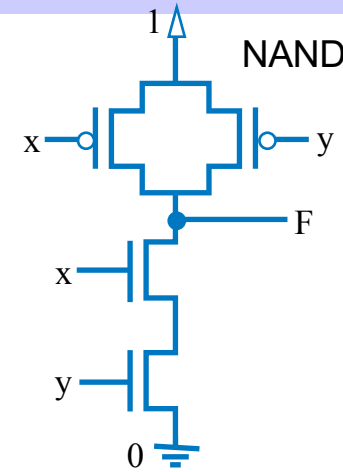
- NAND: Opposite of AND (“NOT AND”)
- NOR: Opposite of OR (“NOT OR”)
- XOR: outputs 1 when inputs have odd number of 1’s
- XNOR: Opposite of XOR (“NOT XOR”)



- AND in CMOS: NAND with NOT
- OR in CMOS: NOR with NOT
- So NAND/NOR more common

Detecting Overflow: Method 2

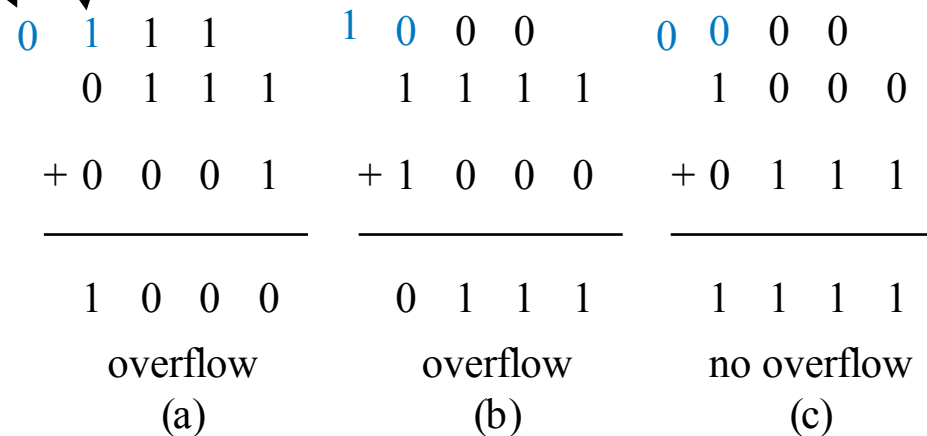
- **Simpler method: Detect difference between carry-in to sign bit and carry-out from sign bit**
- **$\text{overflow} = c_4 \oplus c_3$**




If the carry into the sign bit column differs from the carry out of that column, overflow has occurred.

Gates with Multiple Inputs

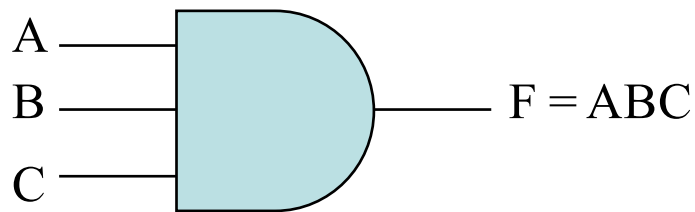- **AND** and **OR** gates may have more than two inputs
- **Three-input AND** gate responds with logic 1 output if and only if all three inputs are logic 1 (may be generalized)
- **Four-input OR** gate responds with logic 1 if any input is logic 1; its output becomes 0 if and only if all inputs are logic 0 (may be generalized)






3-input AND gate

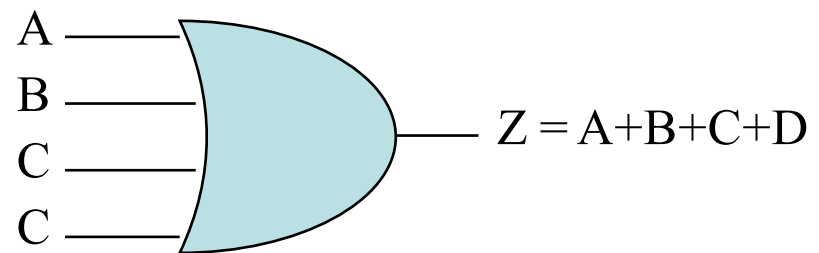

4-input OR gate

Some Circuit Drawing Conventions

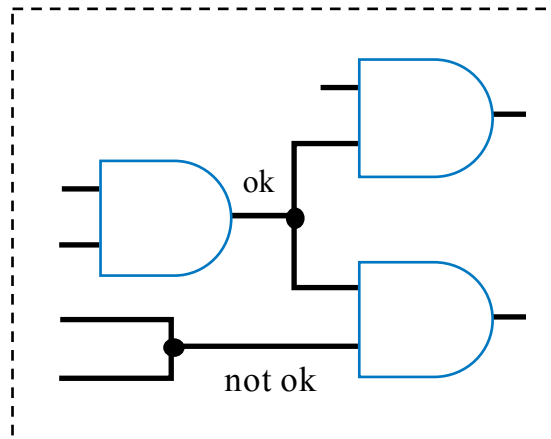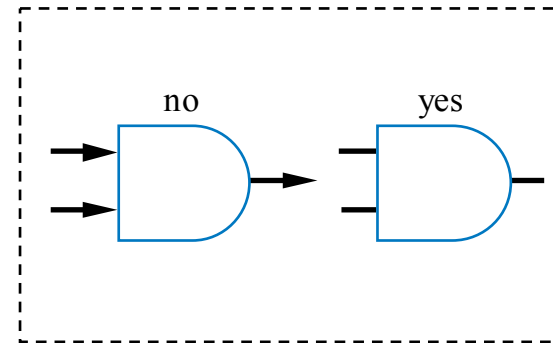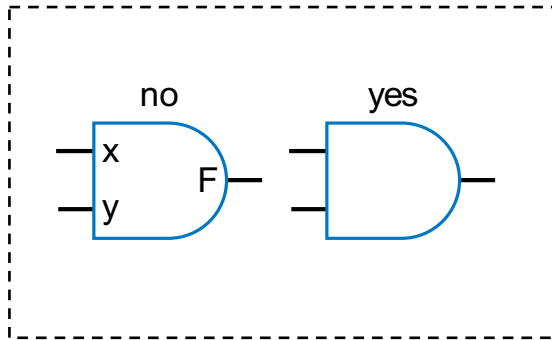


Integrated Circuit

- **Integrated Circuit (IC) – chip**
 - Contains logic components and/or devices for constructing digital circuits
- **Integration Levels**
 - Small-Scale Integration (SSI)
 - Fewer than 10 gates
 - Medium-Scale Integration (MSI)
 - 10 to 1000 gates
 - Large-Scale Integration (LSI)
 - Thousands of gates
 - Very Large-Scale Integration (VLSI)
 - Millions of gates
 - Ultra Large-Scale Integration (ULSI)
 - Billions of gates
 - ...

Integrated Circuit

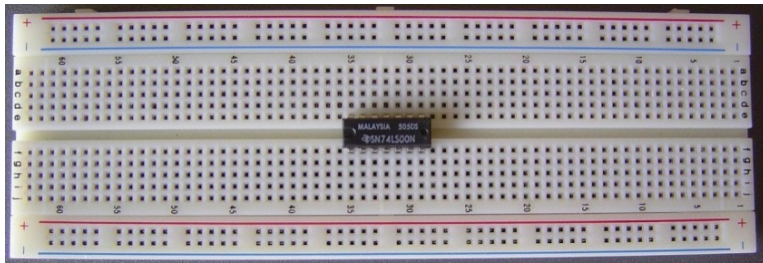- **TTL** – Transistor-Transistor Logic
- **ECL** – Emitter-Coupled Logic
- **MOS** – Metal-Oxide Semiconductor
- **CMOS** – Complementary MOS



Chip placed on breadboard

